

Phasor Representation of AC quantities

$$\Rightarrow v(t) = V_m \sin(\omega t + \phi)$$

$$i(t) = I_m \sin(\omega t + \phi)$$


$v(t)$, $i(t)$ are called instantaneous values $\theta = \omega t \rightarrow \frac{\text{rad}}{\text{sec}} \times \text{sec}$

$V_m, I_m \Rightarrow$ peak values, Amplitude


$\omega \rightarrow$ angular frequency radians/second

$t \rightarrow$ time

$\phi \rightarrow$ initial phase angle

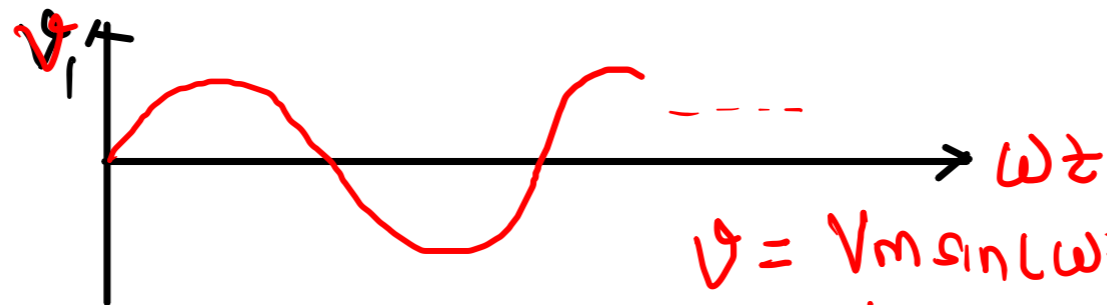
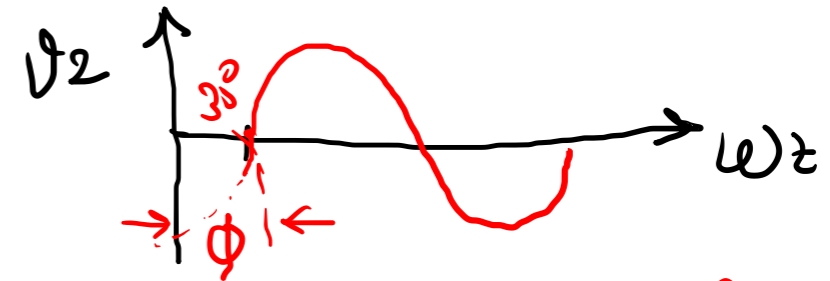
$$v = V_m \sin(\omega t + 0) \\ = V_m \sin(\theta)$$



$$v_2 = V_m \sin(\omega t - \phi)$$

Phasor Representation of AC quantities

$$\Rightarrow v(t) = V_m \sin(\omega t + \phi)$$

$$i(t) = I_m \sin(\omega t + \phi)$$


$v(t)$, $i(t)$ are called instantaneous values $\theta = \omega t \rightarrow \frac{\text{rad}}{\text{sec}} \times \text{sec}$

V_m , $I_m \Rightarrow$ peak values, Amplitude

$\omega \rightarrow$ angular frequency radians/second



$t \rightarrow$ time

$\phi \rightarrow$ initial phase angle

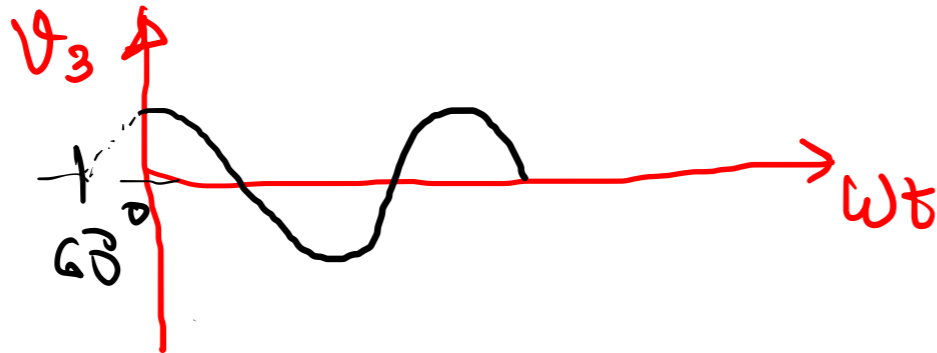

$$v_3 = V_m \sin(\omega t + 60^\circ)$$

Phasor Representation of AC quantities

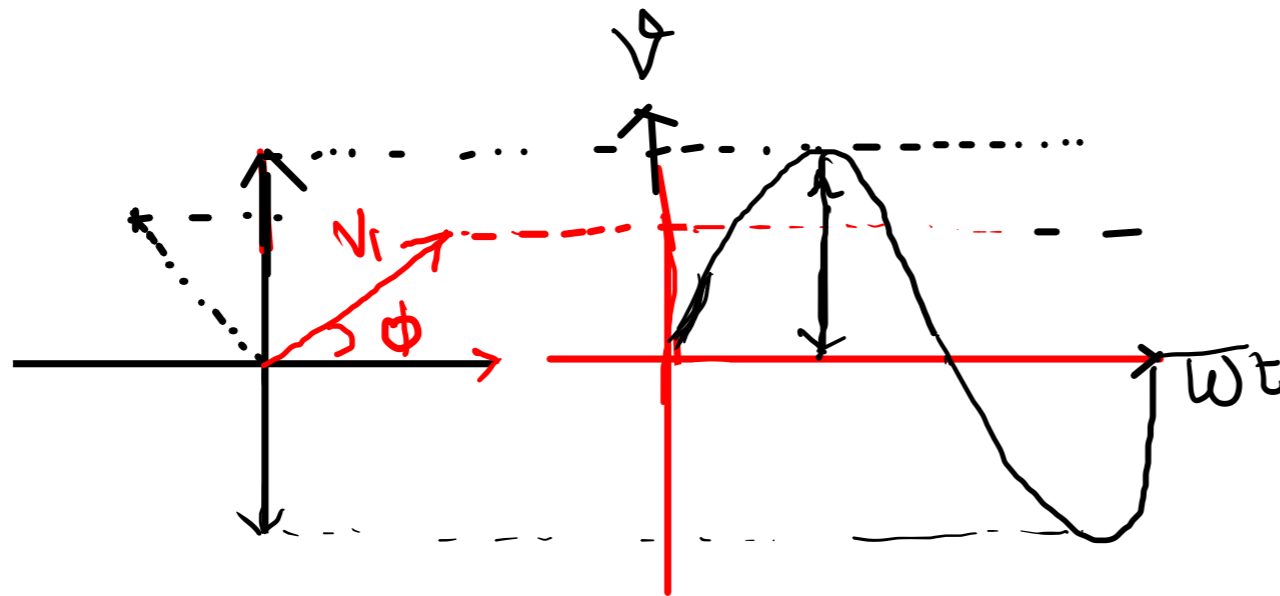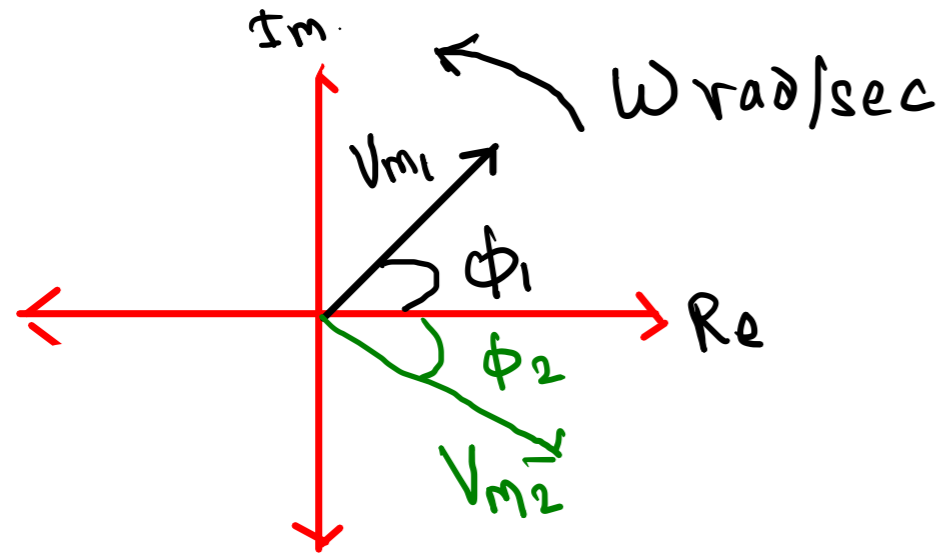

$$v_1 = V_{m1} \sin(\omega t + \phi_1)$$

$$v_2 = V_{m2} \sin(\omega t - \phi_2)$$


$$\left\{ \begin{array}{l} v_1 + v_2 \\ v_2 - v_1 \\ v_1 \neq v_2 \\ \frac{v_1}{v_2} \end{array} \right.$$

Normally rms values
of ac quantities used
in phasor representation

Phasor Representation of AC quantities

⇒ To draw phasor diagram of AC quantities they must have same frequency.

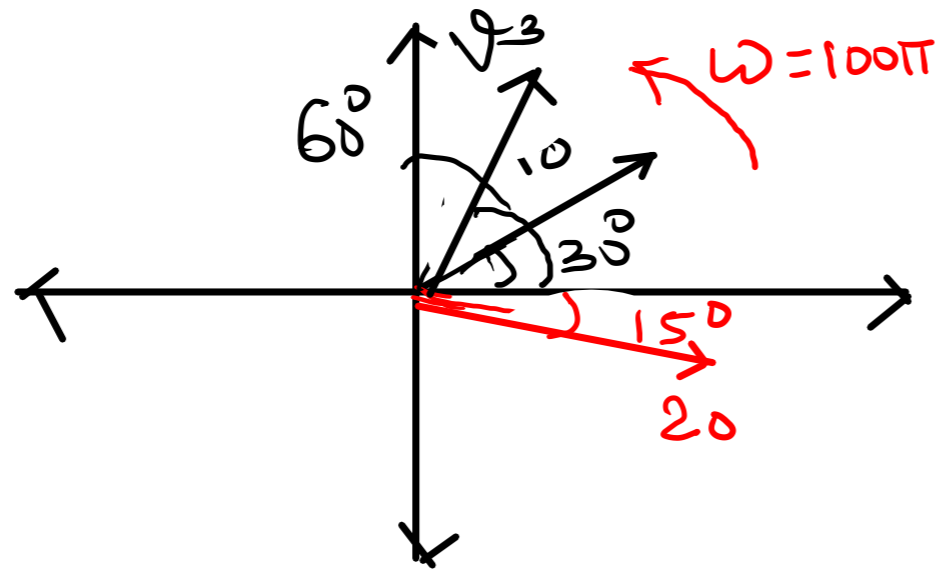⇒ Phasor diagram provides information about phase relation between two AC quantities.



⇒ V_3 leads both i_1 & V_1 .

$$i_1 = 10 \sin(100\pi t + 30^\circ)$$

$$V_1 = 20 \sin(100\pi t - 15^\circ)$$

⇒ Leading & Lagging phasors

→ i_1 is leading V_1 by 45°

V_1 is lagging i_1 by 45°

$$V_3 = 5 \sin(100\pi t + 60^\circ)$$

Phasor Representation of AC quantities

⇒ Mathematical representation of phasors.

$$v = \underline{V_m} \sin(\omega t + \phi)$$

$$v = V_m \angle \phi$$

$$i = I_m \sin(\omega t - \phi)$$



$$i = I_m \angle -\phi$$

Polar form: $r \angle \phi$ $r \rightarrow$ magnitude $\phi =$ angle

Rectangular form $x + jy$ $r = \sqrt{x^2 + y^2}$
 $\phi = \tan^{-1} \left(\frac{y}{x} \right)$

Exponential form: $r e^{j\phi} \Rightarrow (r \cos \phi + j r \sin \phi) :$
 $\downarrow \qquad \qquad \downarrow$
 $x \qquad + j \qquad y$

Phasor Representation of AC quantities

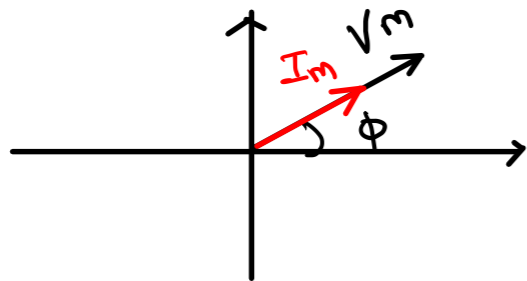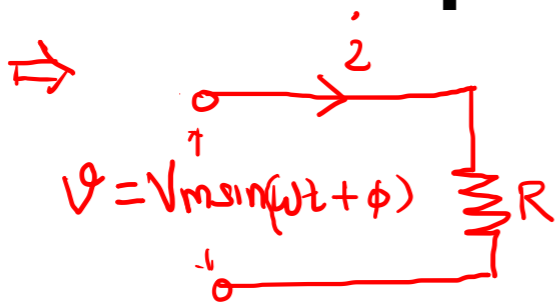




$$i = \frac{V}{R} \text{ (Ohms Law)}$$

$$i = \frac{V_m \sin(\omega t + \phi)}{R}$$

$$i = \frac{V_m}{R} \sin(\omega t + \phi)$$

$$i = I_m \sin(\omega t + \phi)$$

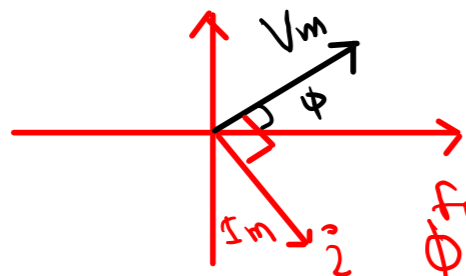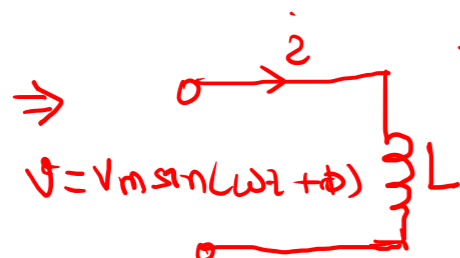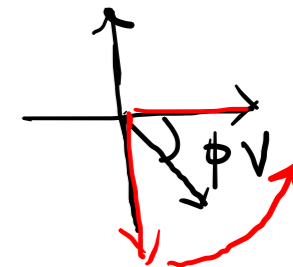V_m & I_m are in phase (no phase difference)




Voltage across(L) Current flowing inductor
 $V_L = L \cdot \frac{di}{dt}$ $I_L = \frac{1}{L} \int V_L dt$

$$i = \frac{1}{L} \int V dt = \frac{1}{L} \int V_m (\sin \omega t + \phi) dt$$

$$i = \frac{V_m}{L} \frac{-\cos(\omega t + \phi)}{\omega} = \frac{V_m}{\omega L} [-\cos(\omega t + \phi)]$$
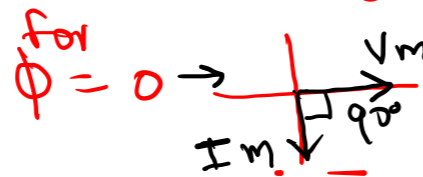
$$i = \frac{V_m}{\omega L} \sin(\omega t + \phi - 90^\circ)$$




Current is lagging voltage by 90° .

$$\phi$$

$$P = VI \cos(\phi) \text{ Active power}$$

$$Q = VI \sin(\phi) \text{ Reactive power}$$

Phasor Representation of AC quantities

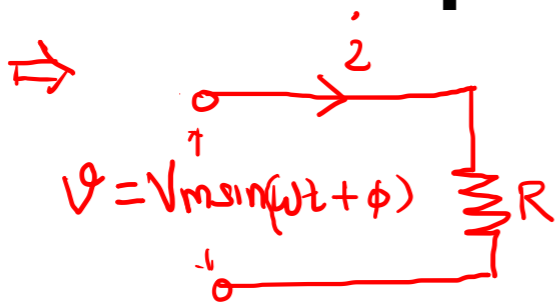


$$i = \frac{V}{R} \text{ (Ohms Law)}$$



$$i = \frac{V_m \sin(\omega t + \phi)}{R}$$

$$i = \frac{V_m}{R} \sin(\omega t + \phi)$$

$$i = I_m \sin(\omega t + \phi)$$

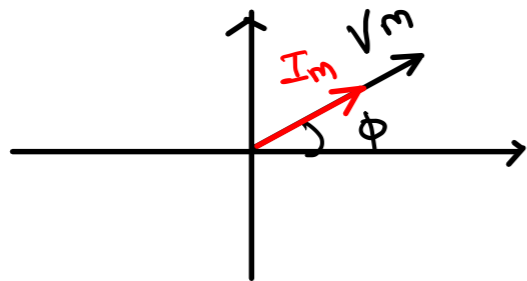

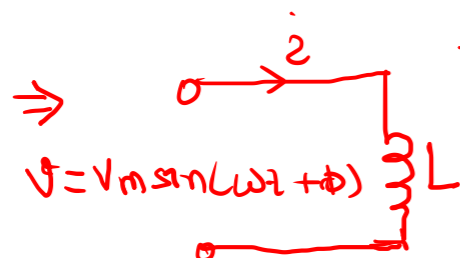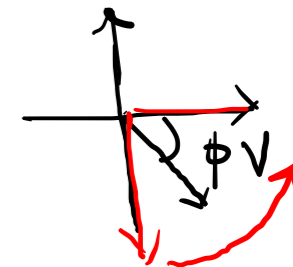V_m & I_m are in phase (no phase difference)




→ Voltage across(L) Current flowing inductor
 $V_L = L \cdot \frac{di}{dt}$ $I_L = \frac{1}{L} \int V_L dt$


$$i = \frac{1}{L} \int V dt = \frac{1}{L} \int V_m (\sin \omega t + \phi) dt$$

$$i = \frac{V_m}{L} \frac{-\cos(\omega t + \phi)}{\omega} = \frac{V_m}{\omega L} [-\cos(\omega t + \phi)]$$
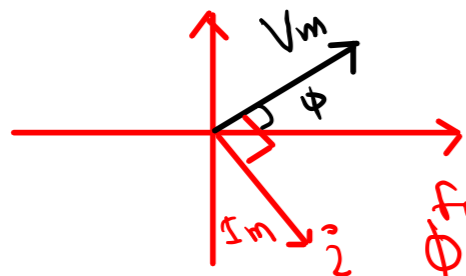
$$i = \frac{V_m}{\omega L} \sin(\omega t + \phi - 90^\circ)$$



for $\phi = 0$

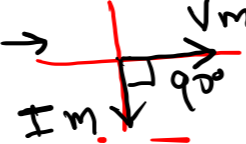


Current is lagging voltage by 90° .

$$\phi$$

$P = VI \cos(\phi)$ Active power
 $Q = VI \sin(\phi)$ Reactive power

Phasor Representation of AC quantities

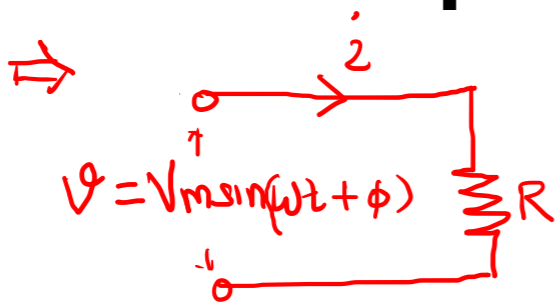


$$i = \frac{V}{R} \text{ (Ohms Law)}$$



$$i = \frac{V_m \sin(\omega t + \phi)}{R}$$

$$i = \frac{V_m}{R} \sin(\omega t + \phi)$$

$$i = I_m \sin(\omega t + \phi)$$

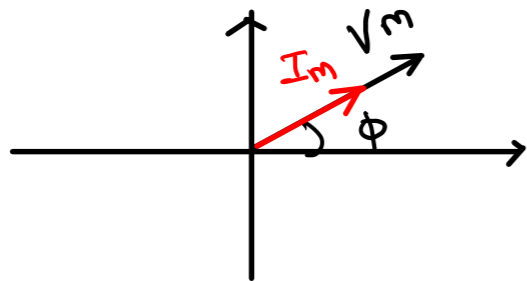

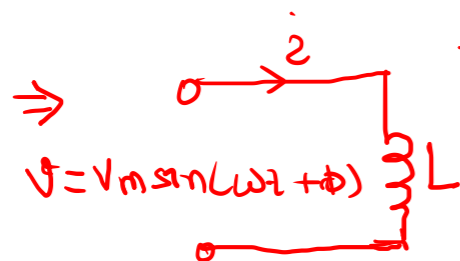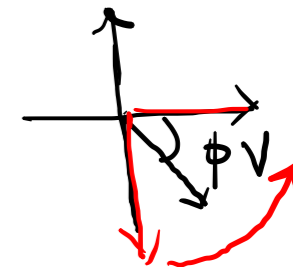V_m & I_m are in phase (no phase difference)




→ Voltage across(L) Current flowing inductor
 $V_L = L \cdot \frac{di}{dt}$ $I_L = \frac{1}{L} \int V_L dt$

$$i = \frac{1}{L} \int V dt = \frac{1}{L} \int V_m (\sin \omega t + \phi) dt$$

$$i = \frac{V_m}{L} \frac{-\cos(\omega t + \phi)}{\omega} = \frac{V_m}{\omega L} [-\cos(\omega t + \phi)]$$
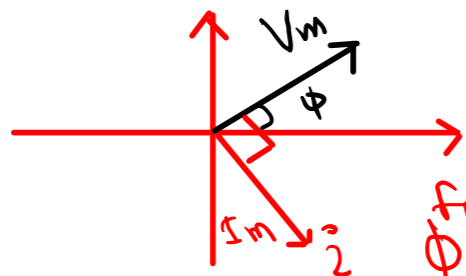
$$i = \frac{V_m}{\omega L} \sin(\omega t + \phi - 90^\circ)$$



for $\phi = 0$




Current is lagging voltage by 90° .

$$\phi$$

$P = VI \cos(\phi)$ Active power
 $Q = VI \sin(\phi)$ Reactive power

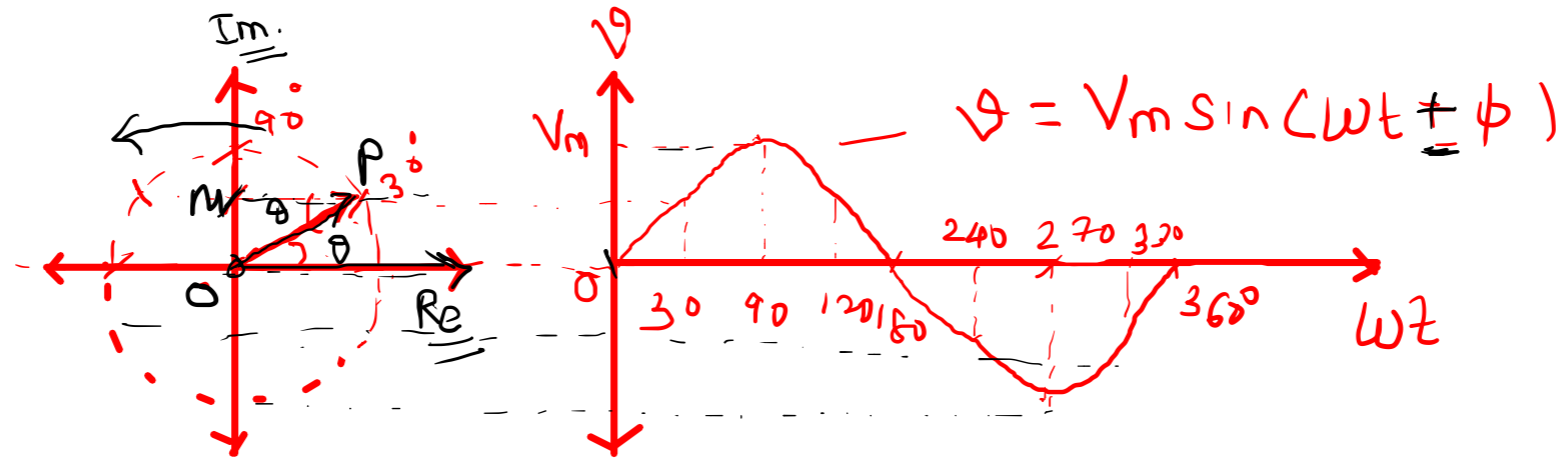Phasor Representation of alternating quantities



$$v = V_m \sin \theta = V_m \sin(\omega t)$$


$$\sin \theta = \frac{OM}{OP} \quad \underline{OM = OP \sin \theta}$$

$$v = V_m \sin(\omega t \pm \phi)$$


$$\leftarrow v_2 = V_m \sin(\omega t - 90^\circ)$$

$$v_3 = V_m \sin(\omega t + 60^\circ)$$

Lagging
Leading

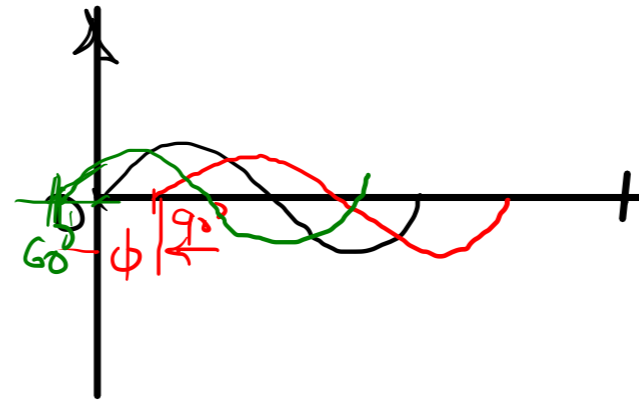


①

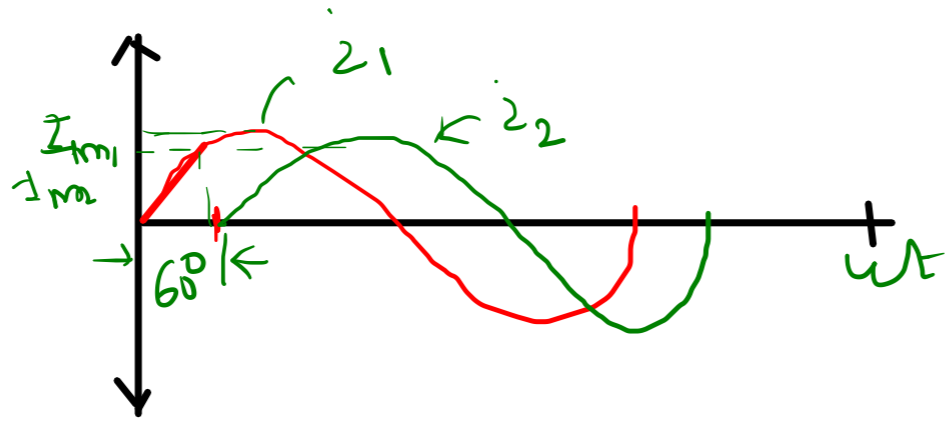

$$i_1 = I_{m1} \sin(\omega t) = |I_{m1}| \angle 0^\circ$$

$$i_2 = I_{m2} \sin(\omega t - 60^\circ) = |I_{m2}| \angle -60^\circ$$

$$i_3 = I_{m3} \sin(\omega t + 45^\circ) = |I_{m3}| \angle 45^\circ$$

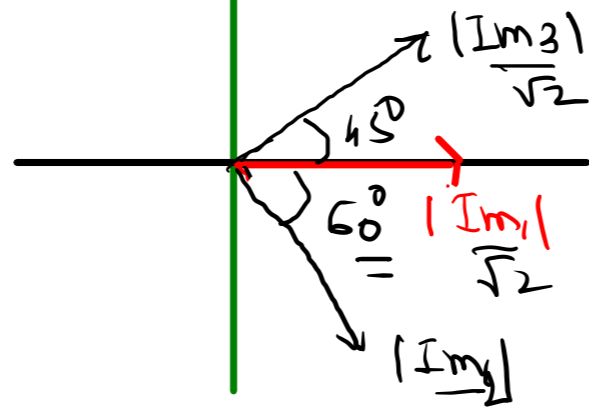

✓ I_{m2} is lagging I_{m1} by 60°

✓ I_{m1} is leading I_{m2} by 60°

length of $\frac{\sqrt{2}}{2}$ is Rms value of alternating quantity
phasor

① Two sinusoidal currents are given as

$$i_1 = 10\sqrt{2} \sin \omega t \quad \& \quad i_2 = 20\sqrt{2} \sin(\omega t + 90^\circ)$$

Find sum of the currents

$$\Rightarrow i_1 + i_2$$

$$i_1 = \frac{10\sqrt{2}}{\sqrt{2}} \angle 0^\circ$$

$$i_2 = \frac{20\sqrt{2}}{\sqrt{2}} \angle 90^\circ$$

$$i_1 = 10 \angle 0^\circ$$

$$i_2 = 20 \angle 90^\circ$$

$$i_1 + i_2 = 10 \angle 0^\circ + 20 \angle 90^\circ$$

$$= 10 \cos 0 + j 10 \sin 0 + 20 \cos 90 + j 20 \sin 90$$

$$= 10 + j 0 + 20 \cdot (0) + j 20 (1)$$

$$i_1 + i_2 = 10 + j 20$$

$$= \sqrt{(10)^2 + (20)^2} \angle \tan^{-1} \left(\frac{20}{10} \right)$$

$$= 22.36 \angle 63.43$$

$$i_1 + i_2 = (22.36) \cdot \sqrt{2} \cdot \sin(\omega t + 63.43)$$

① Two sinusoidal currents are given as

$$i_1 = 10\sqrt{2} \sin \omega t \quad \& \quad i_2 = 20\sqrt{2} \sin(\omega t + 90^\circ)$$

Find sum of the currents


$$\Rightarrow i_1 + i_2$$

$$i_1 = \frac{10\sqrt{2}}{\sqrt{2}} \angle 0^\circ$$


$$i_2 = \frac{20\sqrt{2}}{\sqrt{2}} \angle 90^\circ$$

$$i_1 = 10 \angle 0^\circ$$


$$i_2 = 20 \angle 90^\circ$$

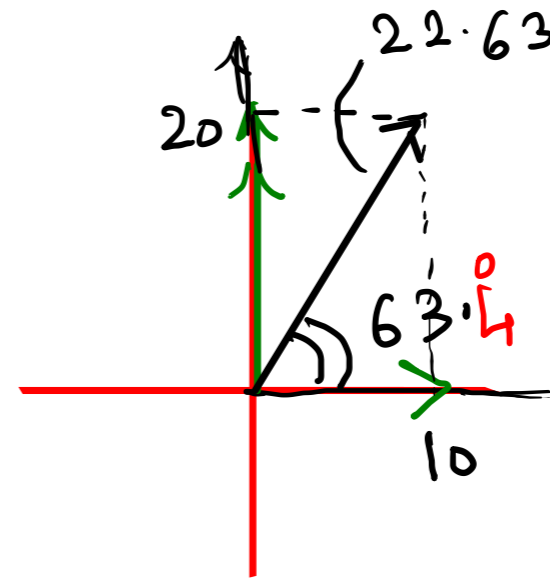

law of
parallelogram

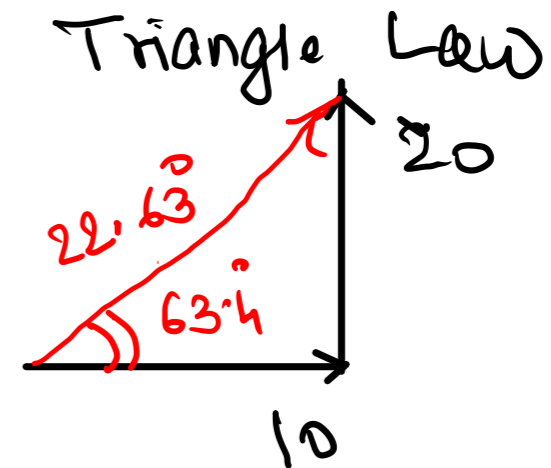


⇒ Response of resistor to AC input.

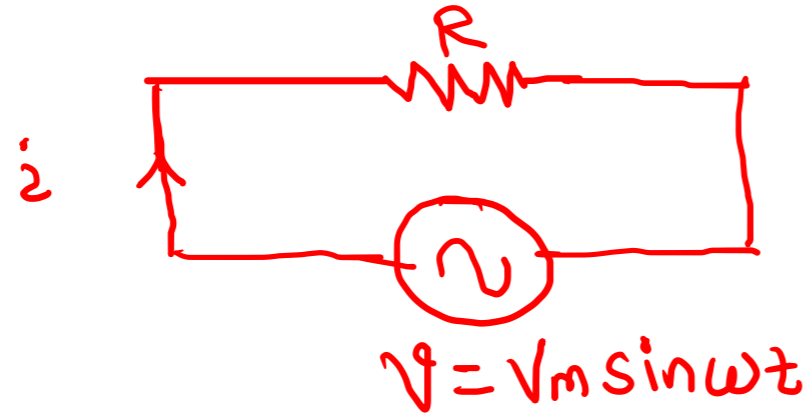

$$\begin{aligned} \Rightarrow i &= \frac{v}{R} \\ i &= \frac{V_m \sin \omega t}{R} \\ i &= \frac{V_m}{R} \sin \omega t \\ i &= I_m \sin \omega t \end{aligned}$$

⇒ phasor diagram

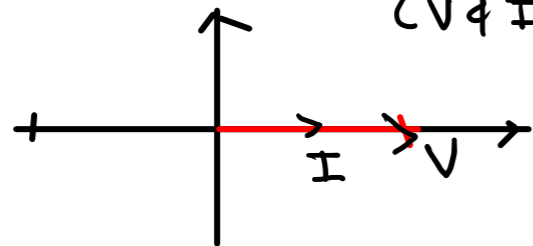

(V & I are rms values)

Voltage and current are in phase

⇒ Impedance of the circuit (Z)

$$Z = \frac{V}{I}, \quad Z = R.$$

⇒ Instantaneous power

$$P_{\text{inst}} = v \cdot i$$


$$P_{\text{inst}} = V_m \sin \omega t \cdot I_m \sin \omega t$$

$$P_{\text{inst}} = V_m I_m \sin^2 \omega t$$

$$P_{\text{inst}} = V_m I_m \left(\frac{1 - \cos 2\omega t}{2} \right)$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$

⇒ Response of resistor to AC input.

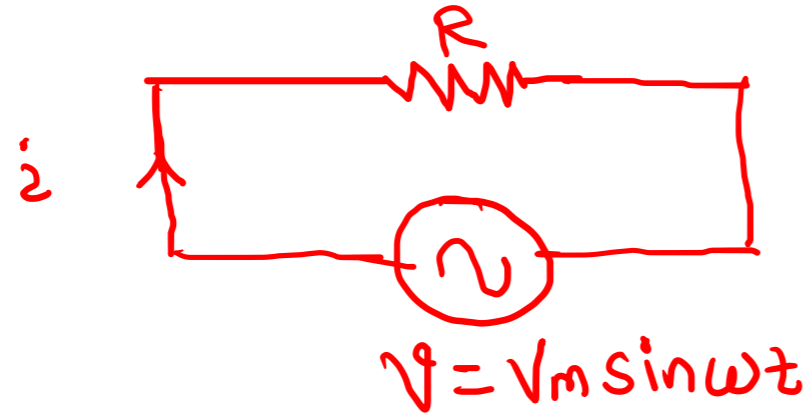

⇒ Instantaneous power

$$P_{inst} = v \cdot i$$


$$P_{inst} = V_m \sin \omega t \cdot I_m \sin \omega t$$

$$P_{inst} = V_m I_m \sin^2 \omega t$$


$$P_{inst} = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$
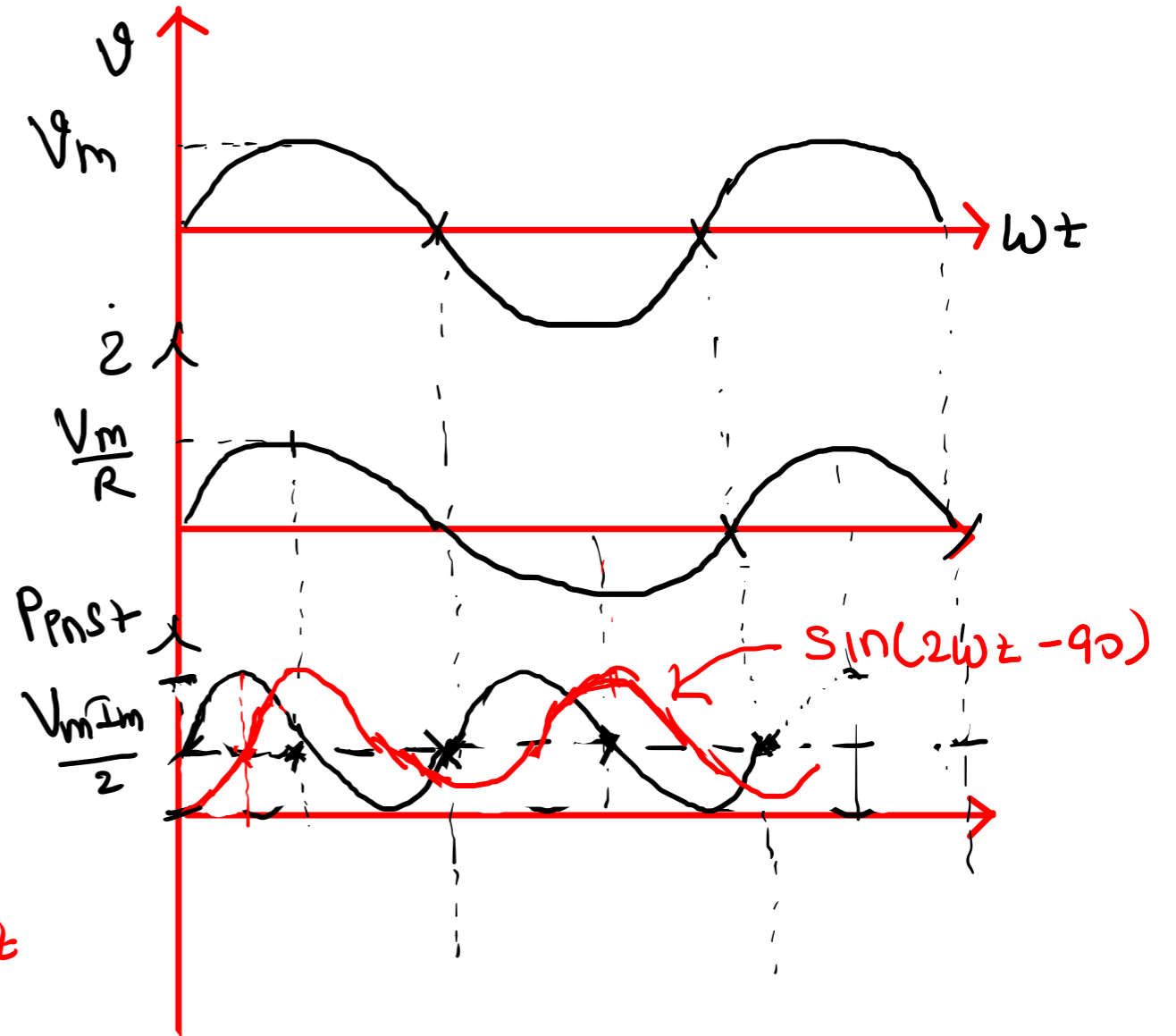
$$= \frac{V_m I_m}{2} + \frac{V_m I_m}{2} \sin(2\omega t - 90)$$



⇒ Response of resistor to AC input.

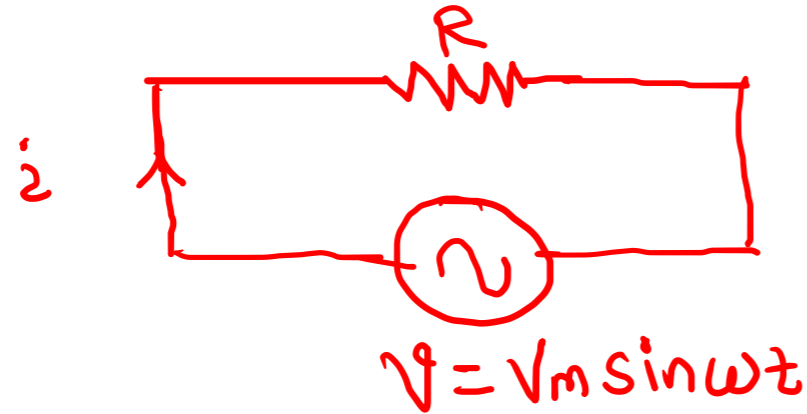

⇒ Instantaneous power

$$P_{inst} = v \cdot i$$


$$P_{inst} = V_m \sin \omega t \cdot I_m \sin \omega t$$

$$P_{inst} = V_m I_m \sin^2 \omega t$$


$$P_{inst} = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$
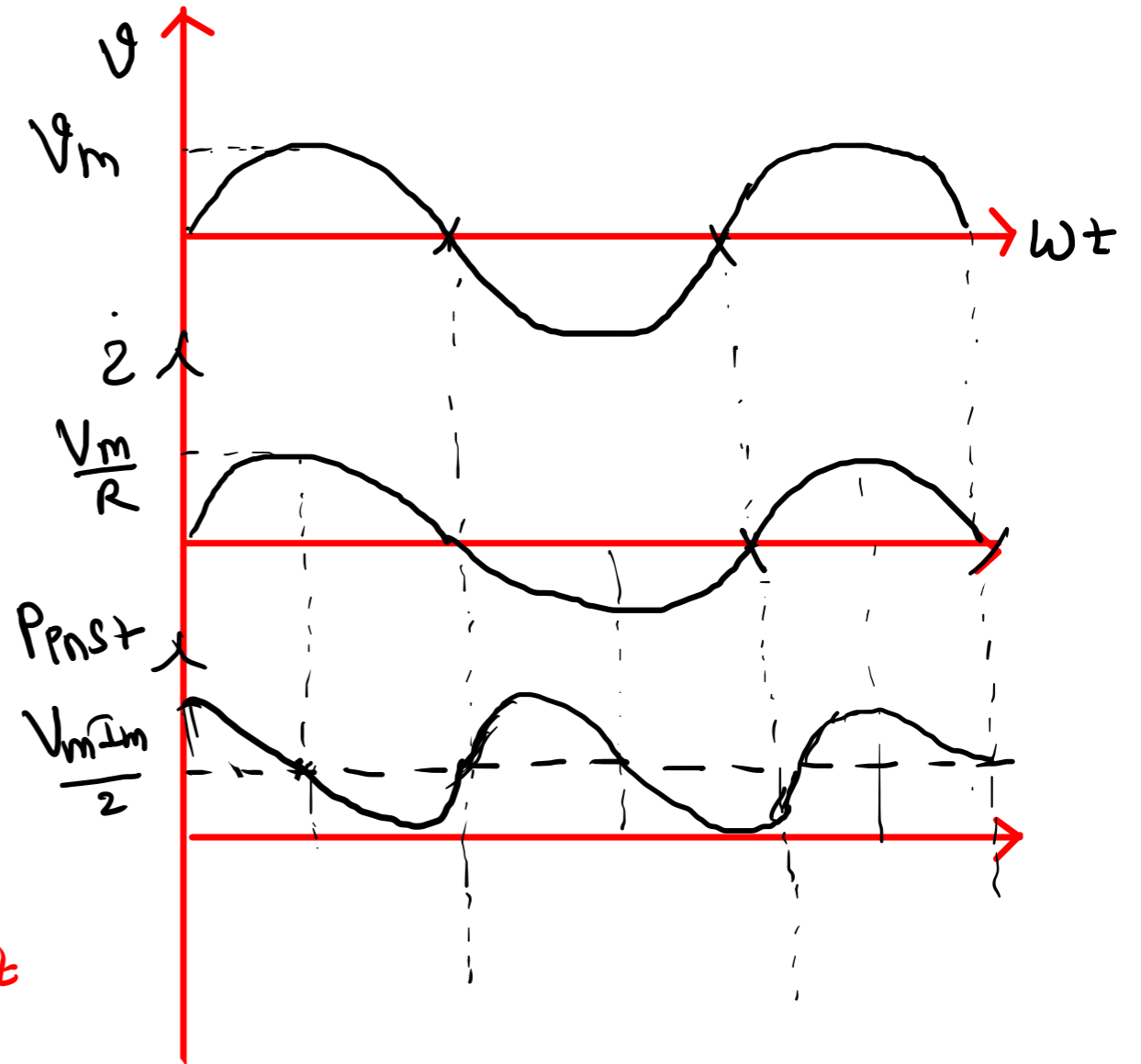
$$= \frac{V_m I_m}{2} + \frac{V_m I_m}{2} \sin(2\omega t - 90)$$



⇒ Response of resistor to AC input.

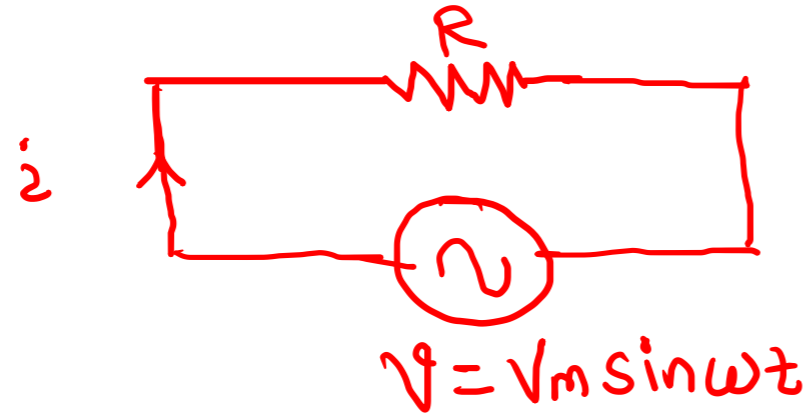

⇒ Instantaneous power


$$P_{inst} = v \cdot i$$

$$P_{inst} = V_m \sin \omega t \cdot I_m \sin \omega t$$

$$P_{inst} = V_m I_m \sin^2 \omega t$$

$$P_{inst} = V_m I_m \left(\frac{1 - \cos 2\omega t}{2} \right)$$
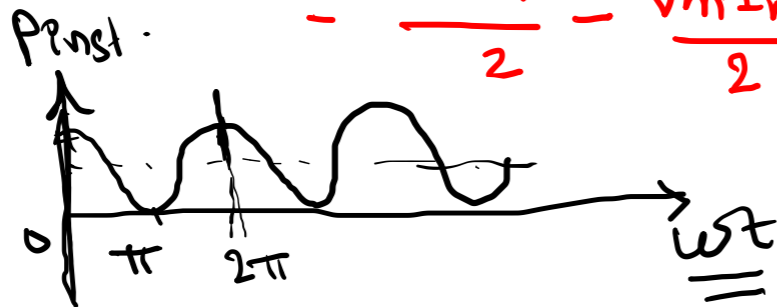
$$= \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$



⇒ Average power (P)

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} P_{inst} \cdot d\omega t$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m I_m \cdot \sin^2 \omega t \cdot d\omega t$$

$$P_{av} = \frac{V_m I_m}{2\pi} \int_0^{2\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t$$


$$P_{av} = \frac{V_m I_m}{2\pi \cdot 2} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{2\pi}$$

$$P_{av} = \frac{V_m I_m}{2 \cdot 2\pi} \left[2\pi - \frac{\sin 4\pi}{2} - 0 - \sin 0 \right]$$

$$P_{av} = \frac{V_m I_m}{2\pi \cdot 2} [2\pi] = \frac{V_m I_m}{2}$$

$$P_{av} = \frac{V_m \cdot I_m}{\sqrt{2} \cdot \sqrt{2}} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{rms} \cdot I_{rms}$$

Response of Pure inductor to AC input

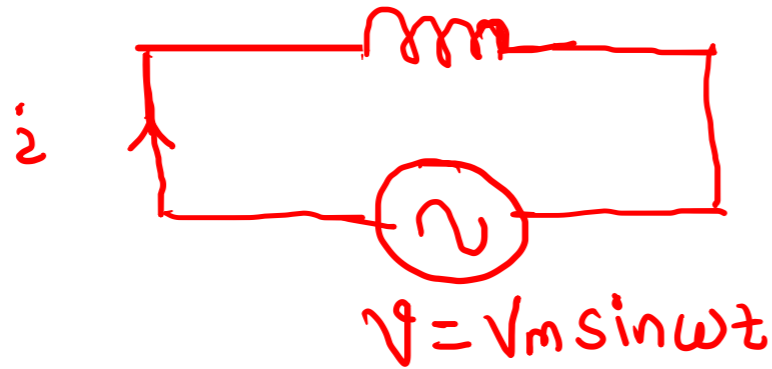

$$\Rightarrow I_L = \frac{1}{L} \int V_L dt, \quad V_L = L \cdot \frac{di_L}{dt}$$

$$i = \frac{1}{L} \int V \cdot dt$$

$$= \frac{1}{L} \int V_m \sin \omega t \cdot dt$$

$$= \frac{V_m}{L} \left[-\frac{\cos \omega t}{\omega} \right]$$

$$i = \frac{V_m}{\omega L} (-\cos \omega t) = -I_m \cos \omega t$$

$$i = \frac{V_m}{\omega L} \sin(\omega t - 90^\circ)$$

$$i = \underline{I_m} \cdot \sin(\omega t - 90^\circ)$$

$$I_m = \frac{V_m}{\omega L}$$


$$\omega L = \frac{V_m}{I_m} = X_L \text{ (Inductive reactance)}$$

$$X_L = \omega L = 2\pi f L$$

for DC
 $f=0, X_L=0$


inductor short for DC

⇒ Phasor diagram

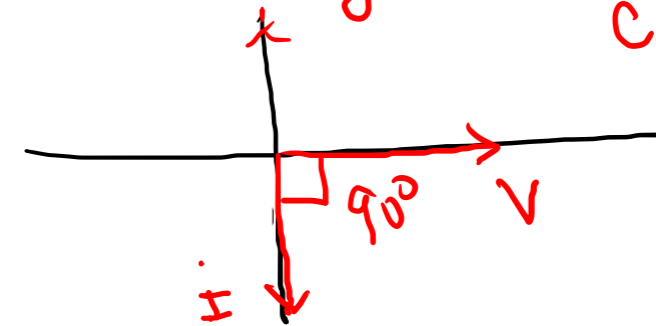


Current is lagging voltage by 90° .

Response of Pure inductor to AC input

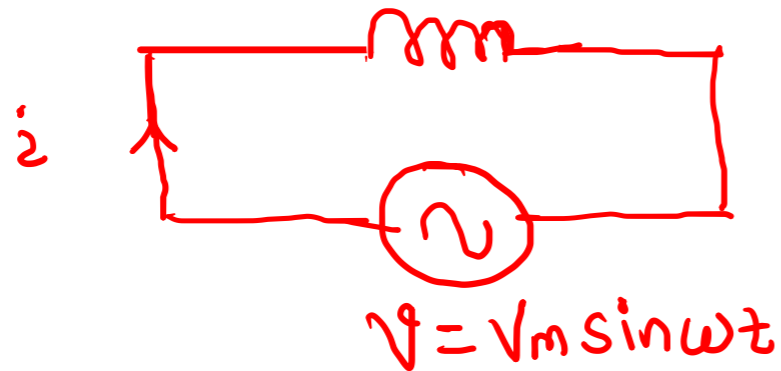

$$\begin{aligned} P_{inst} &= v \cdot i \\ &= (V_m \sin \omega t) \cdot (-I_m \cos \omega t) \\ &= -V_m I_m \sin \omega t \cdot \cos \omega t \end{aligned}$$
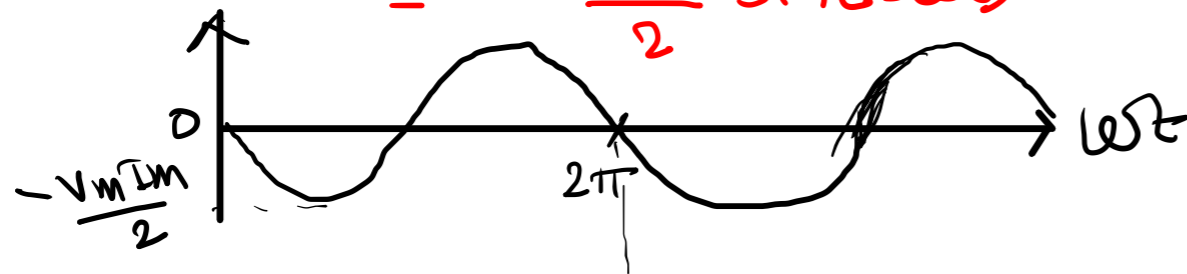
$$\begin{aligned} P_{inst} &= -\frac{V_m I_m \sin(2\omega t)}{2} \\ &= -\frac{V_m I_m \sin(2\omega t)}{2} \end{aligned}$$





$$\begin{aligned} P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} P_{inst} d\omega t \\ &= \frac{1}{2\pi} \int_0^{2\pi} \left(-\frac{V_m I_m}{2} \right) \sin(2\omega t) d\omega t \\ &= -\frac{V_m I_m}{4\pi} \left[-\frac{\cos(2\omega t)}{2} \right]_0^{2\pi} \\ &= -\frac{V_m I_m}{8\pi} [-\cos 4\pi + \cos 0] \\ &= -\frac{V_m I_m}{8\pi} (-1 + 1) \end{aligned}$$


$$P_{av} = 0$$

Average power consumed by pure inductor is zero.

Response of Pure inductor to AC input

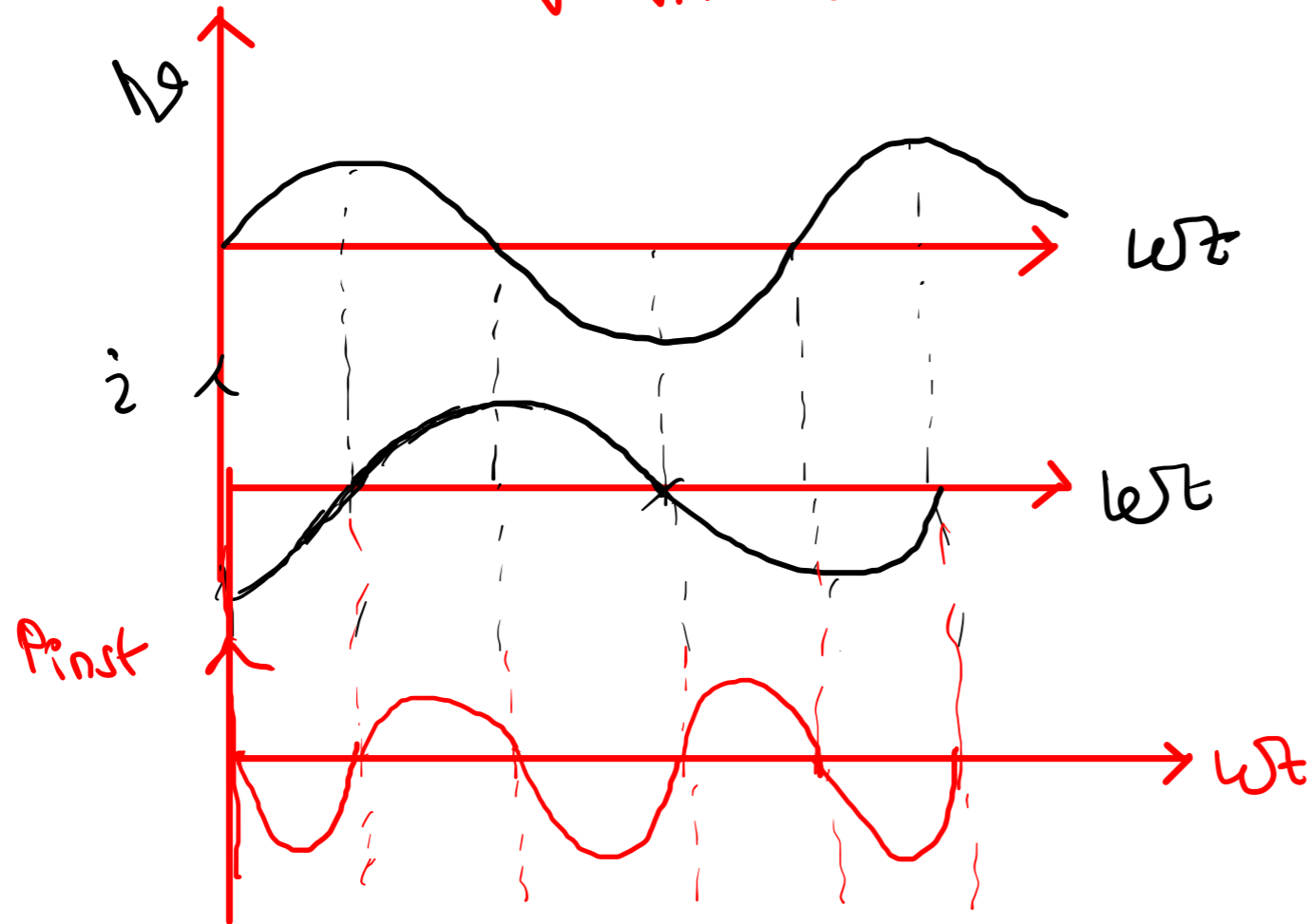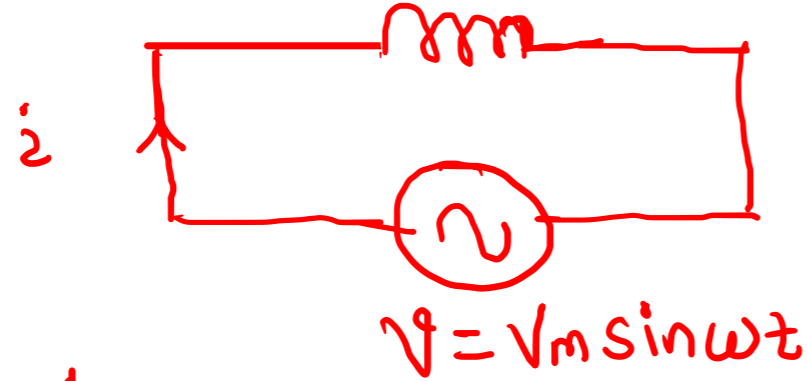

Response of Pure Capacitor to AC input

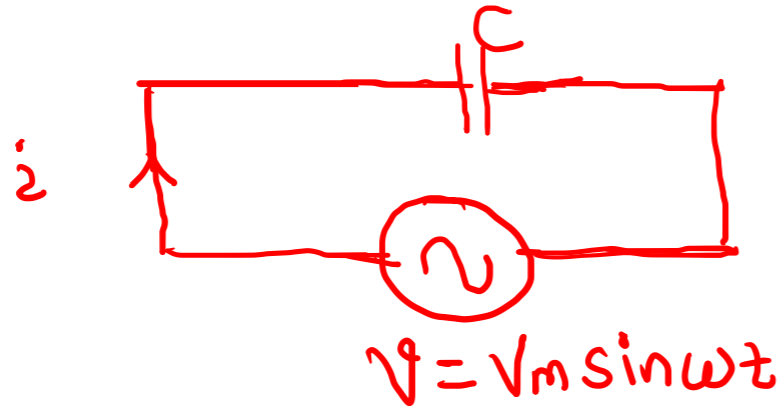

⇒ For capacitor

$$I_c = C \cdot \frac{dv_c}{dt}, \quad v_c = \frac{1}{C} \int I_c dt$$

$$\begin{aligned} i &= C \cdot \frac{dv}{dt} \\ &= C \cdot \frac{d(V_m \sin \omega t)}{dt} \\ &= V_m \cdot C \cdot (\cos \omega t) \cdot \omega \end{aligned}$$

$$i = V_m \cdot \omega C \cos \omega t$$

$$i = I_m \cos \omega t$$

$$I_m = V_m \cdot \omega C = \frac{V_m}{1/\omega C}$$


$$\frac{V_m}{I_m} = \frac{1}{\omega C} \Rightarrow \text{Capacitive Reactance.}$$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$f = 0 \Rightarrow$ For DC input

$X_c = \infty \rightarrow$ open circuit for DC

Response of Pure Capacitor to AC input

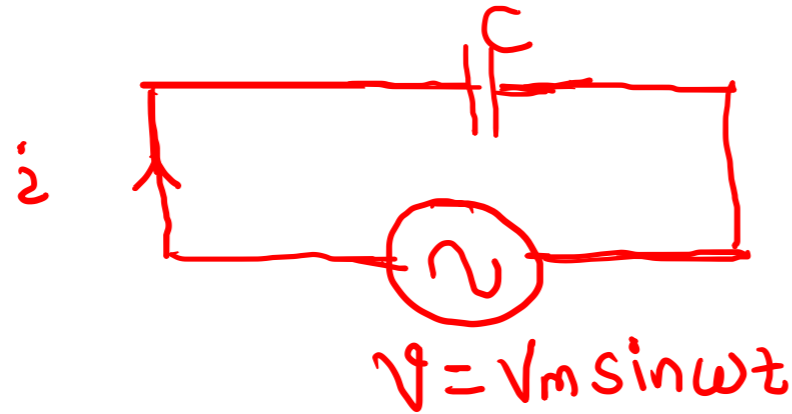

⇒ For capacitor

$$I_c = C \cdot \frac{dV_c}{dt}, \quad V_c = \frac{1}{C} \int I_c dt$$

$$i = C \cdot \frac{dV}{dt}$$


$$= C \cdot \frac{d(V_m \sin \omega t)}{dt}$$

$$= V_m \cdot C \cdot (\cos \omega t) \cdot \omega = I_m \sin(\omega t + \varphi)$$

$$V = V_m \angle 0^\circ$$


$$I = I_m \angle +90^\circ$$

⇒ phasor diagram

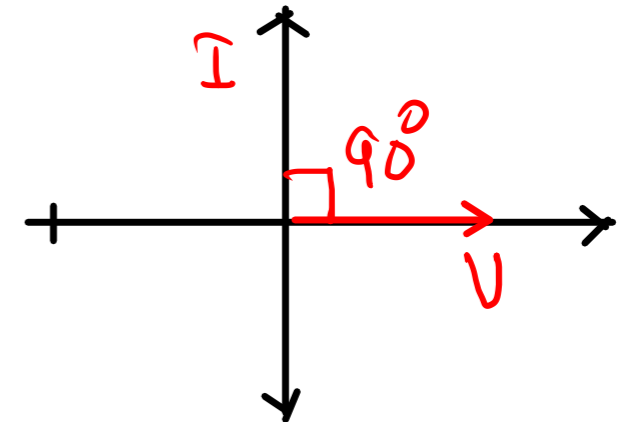

Current leads voltage by 90° .

Reponse of Pure Capacitor to AC input

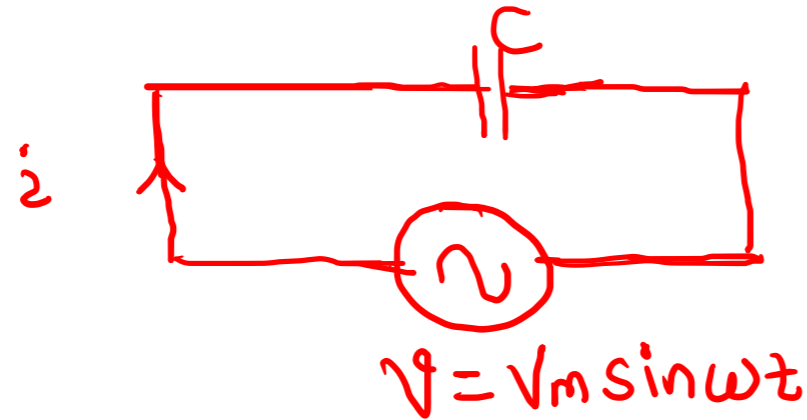


$$V = V_m \sin \omega t$$

$$P_{inst} = V \cdot i$$

$$= V_m \sin \omega t \cdot I_m \cos \omega t$$

$$= V_m I_m \frac{\sin(2\omega t)}{2}$$
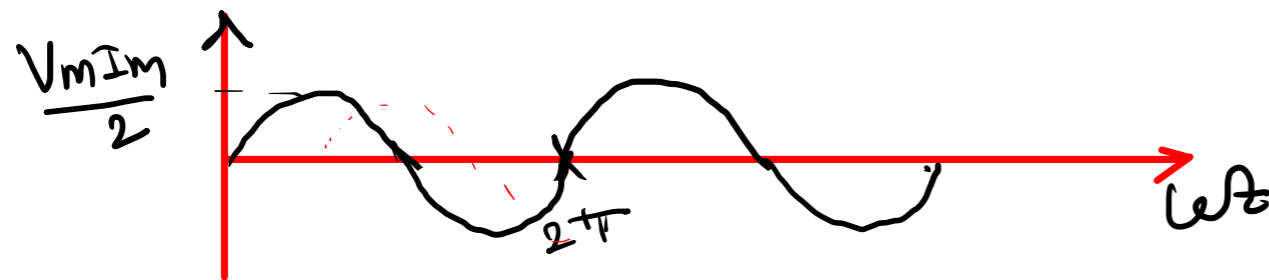
$$P_{inst} = \frac{V_m I_m}{2} \sin(2\omega t)$$



$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \sin(2\omega t) d\omega t$$


$$P_{av} = \frac{V_m I_m}{4\pi} \left[-\frac{\cos 2\omega t}{2} \right]_0^{2\pi}$$

$$= -\frac{V_m I_m}{8\pi} [\cos 4\pi - \cos 0]$$


$$P_{av} = -\frac{V_m I_m}{8\pi} [1 - 1]$$

$$P_{av} = 0$$


Response of Pure Capacitor to AC input

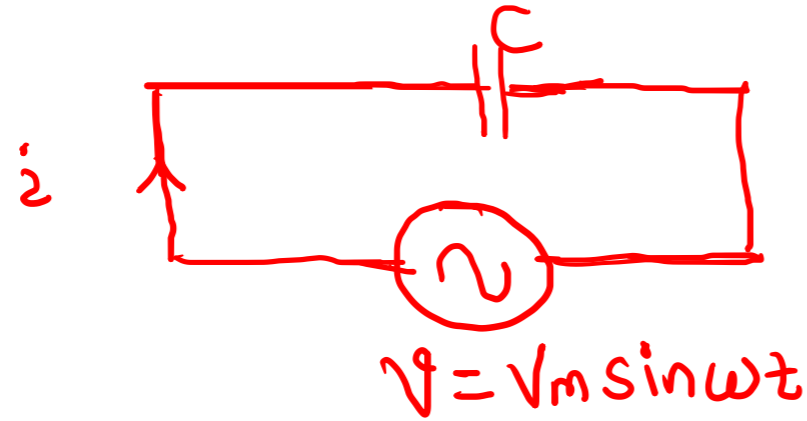


$$v = V_m \sin \omega t$$

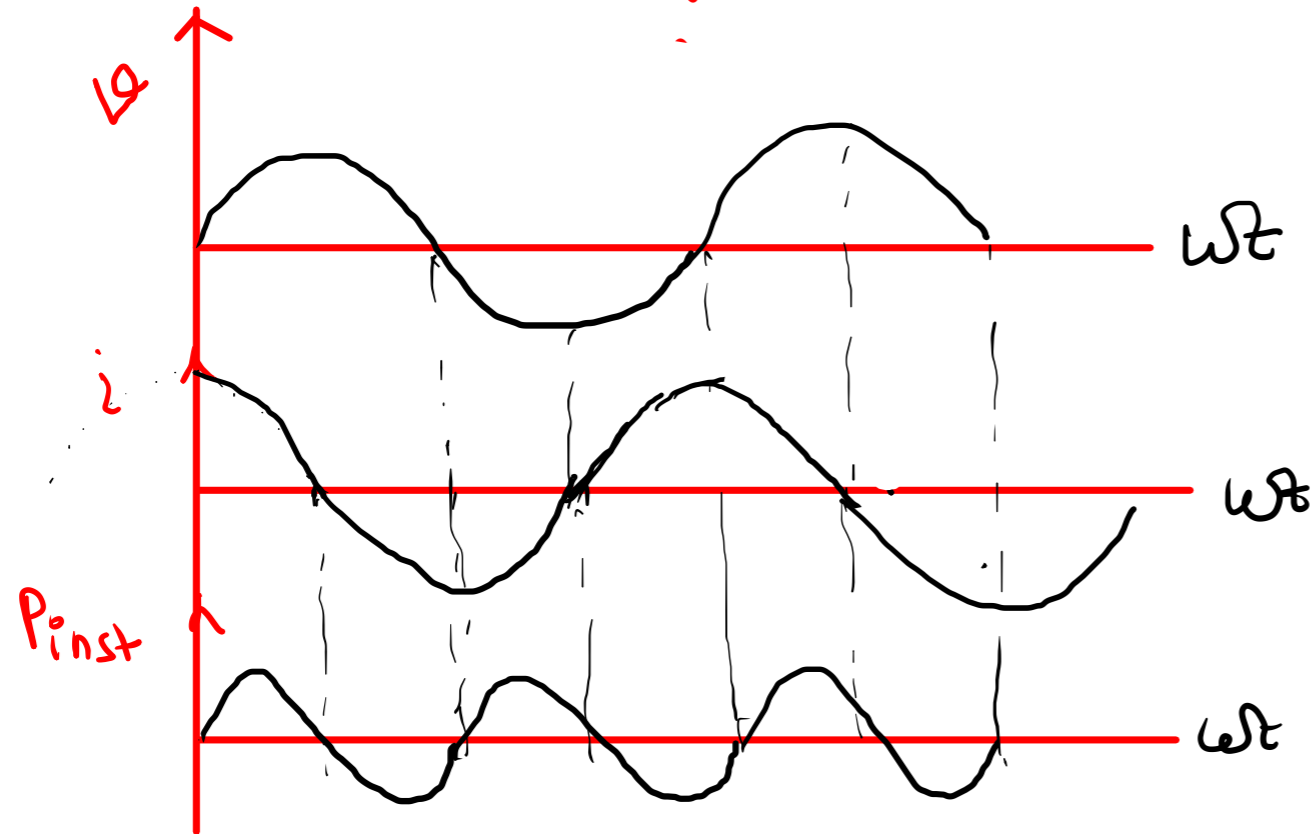

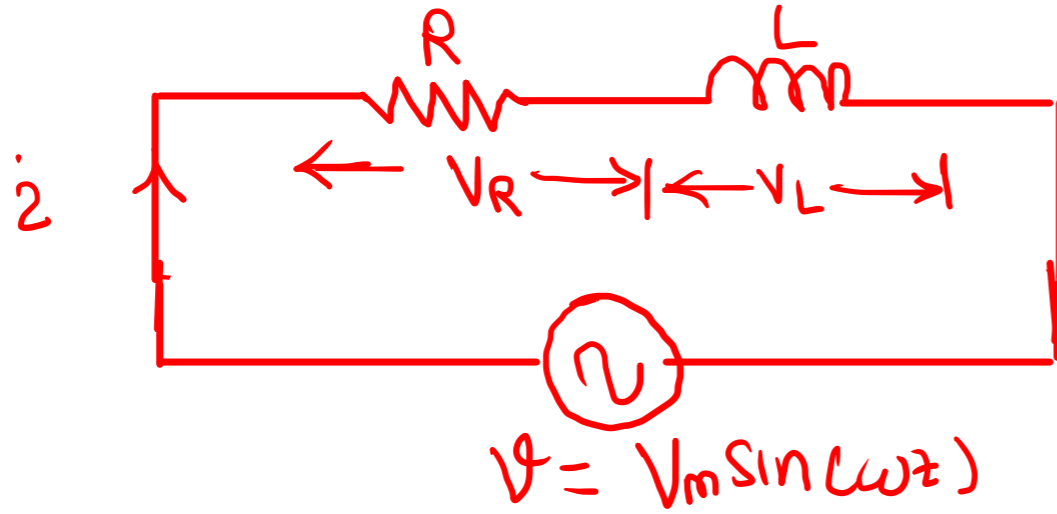Response of Resistor and Inductor series combination to ac input



⇒ phasor diagram.

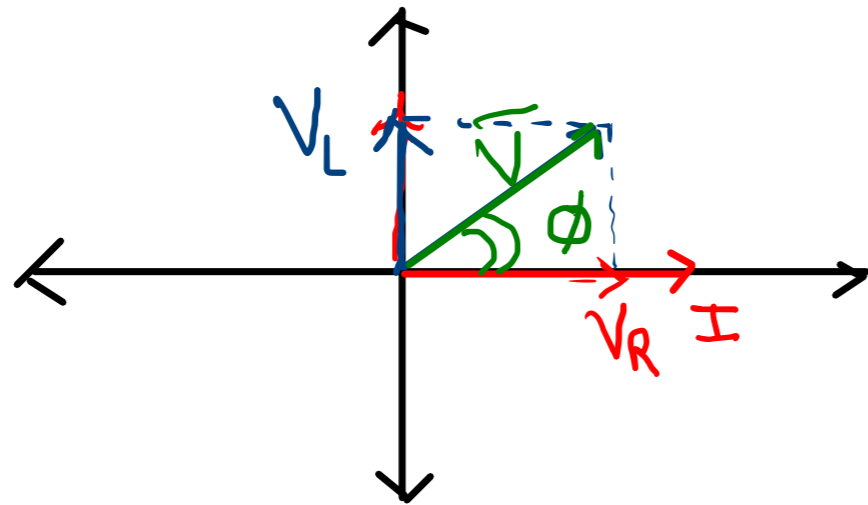

$$\vec{V}_R + \vec{V}_L = \vec{V}$$


⇒ angle between applied & resultant current is ϕ

⇒ voltage (V) leads the current I by ϕ .

⇒ V_R, V_L, V, I are rms values


$$\left. \begin{aligned} V &= V_m \sin \omega t \\ i &= I_m \sin(\omega t - \phi) \end{aligned} \right\}$$

⇒ using triangle Law of vectors.

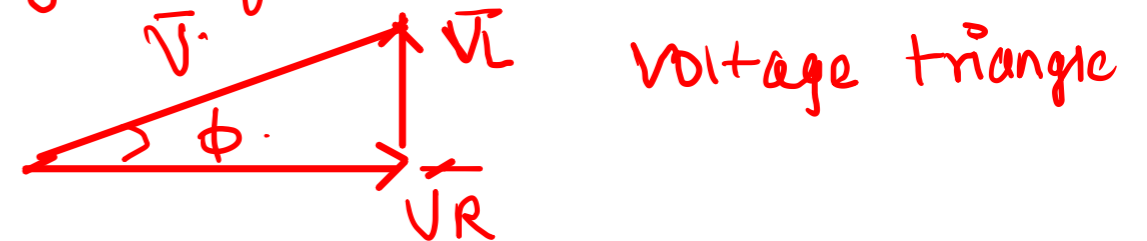


Response of Resistor and Inductor series combination to ac input

(R-L series circuit)

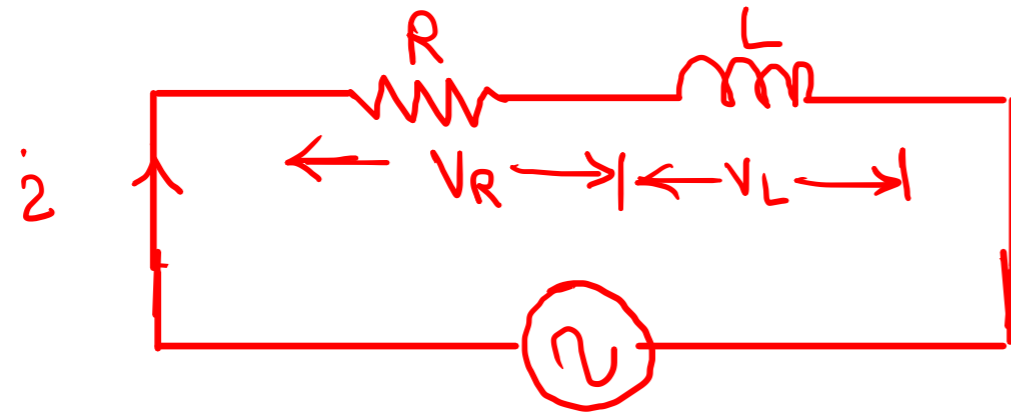


$$V = V_m \sin(\omega t)$$

⇒ using triangle Law of vectors.

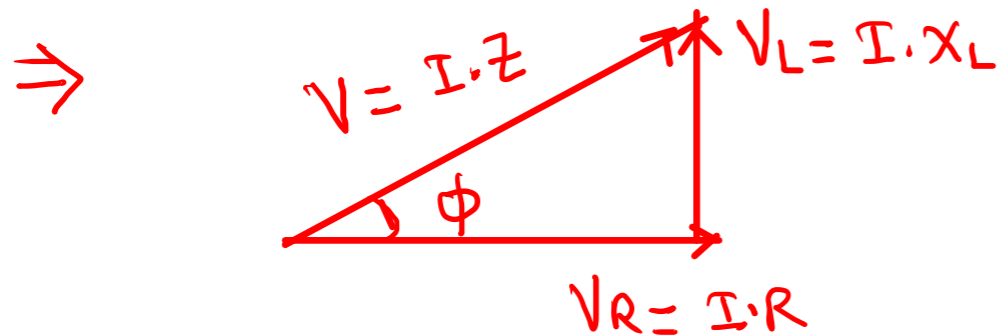

$$\vec{V}_R + \vec{V}_L = \vec{V}$$

⇒

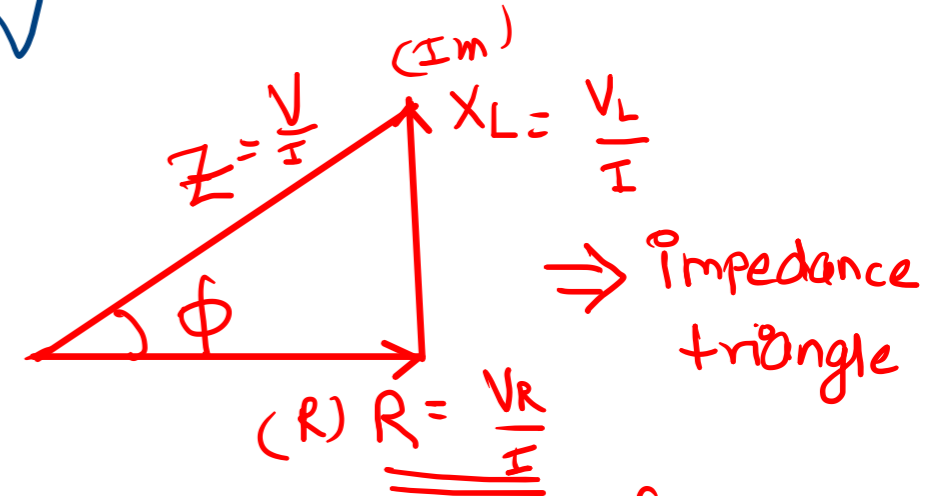


$Z = R + jX_L$ for R-L Series circuit

$$|Z| = \sqrt{R^2 + X_L^2}$$

$$\phi_Z = \tan^{-1} \left(\frac{X_L}{R} \right)$$


Response of Resistor and Inductor series combination to ac input

(R-L series circuit)

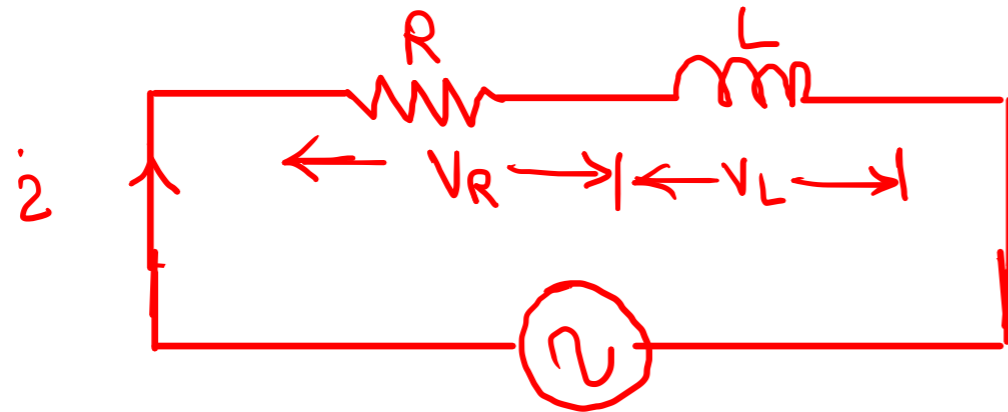


$$V = V_m \sin(\omega t)$$

⇒ using triangle Law of vectors.

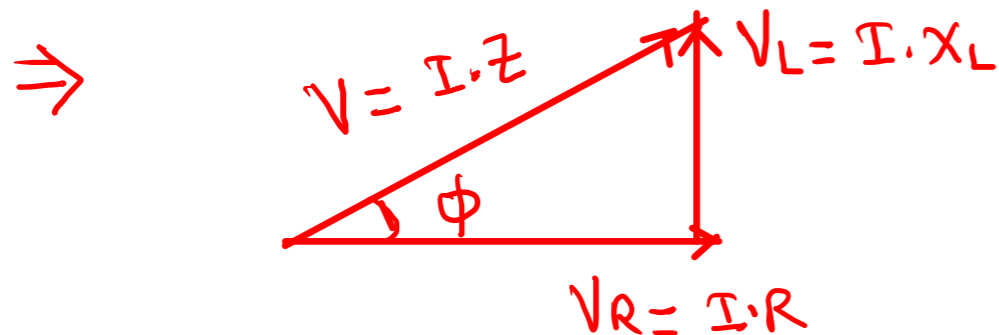

$$\vec{V}_R + \vec{V}_L = \vec{V}$$

⇒

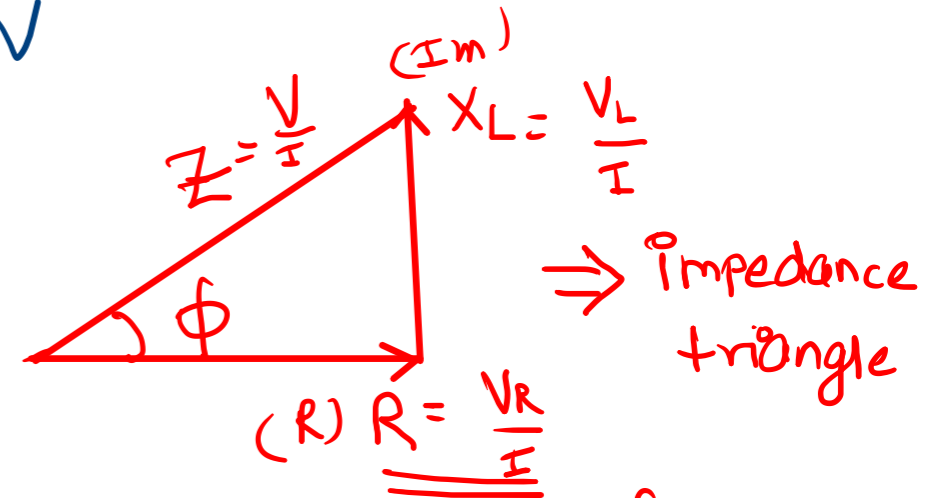


$Z = R + jX_L$ for R-L Series circuit

$$|Z| = \sqrt{R^2 + X_L^2}$$

$$\phi_z = \tan^{-1} \left(\frac{X_L}{R} \right)$$

Response of Resistor and Inductor series combination to ac input

(R-L series circuit)

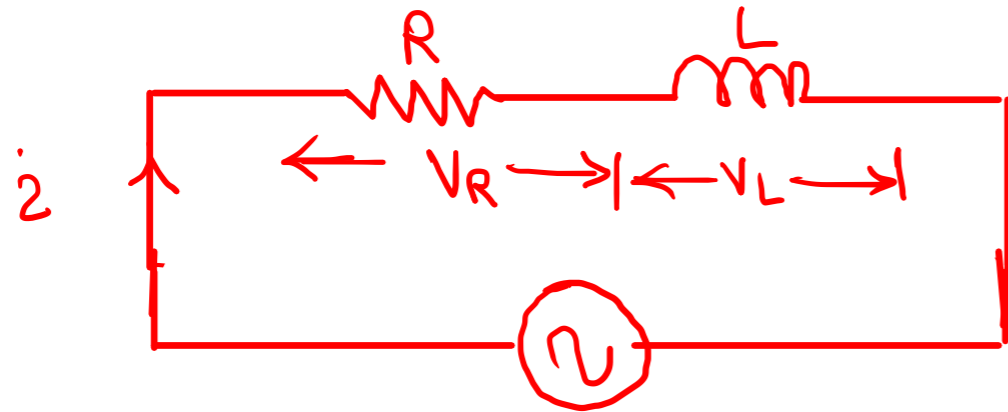

$$v = V_m \sin(\omega t)$$

$$\Rightarrow P_{inst} = v \cdot i$$

$$= V_m \sin \omega t \cdot I_m \sin(\omega t - \phi)$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t - \phi)$$

$$= \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \phi) - \cos(2\omega t - \phi)]$$


$$= \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t - \phi)]$$

$$P_{inst} = \underline{\underline{\frac{V_m I_m}{2} \cos \phi}} - \frac{V_m I_m}{2} \cos(2\omega t - \phi)$$

using
 $\left. \begin{aligned} & \sin A \cdot \sin B \\ &= \cos(A-B) \end{aligned} \right\}$

$$- \cos(A+B)$$

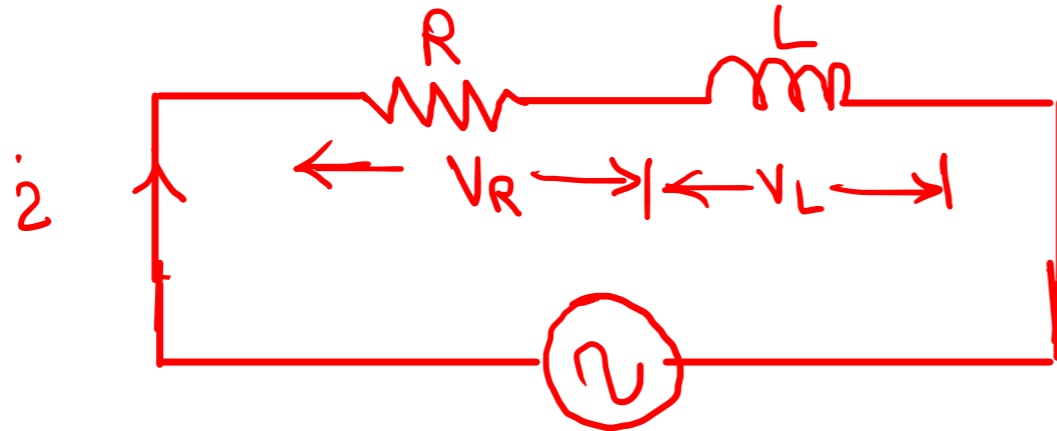Response of Resistor and Inductor series combination to ac input



$$V = V_m \sin(\omega t)$$

$$\begin{aligned}
 P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} P_{inst} \cdot d\omega t \\
 &= \frac{1}{2\pi} \int_0^{2\pi} \left[\frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m \sin 2\omega t}{2} \cos(2\omega t - \phi) \right] d\omega t \\
 &= \frac{1}{2\pi} \left[\frac{V_m I_m}{2} \cos \phi (\omega t) - \frac{V_m I_m}{2} \frac{\sin(2\omega t - \phi)}{2} \right]_0^{2\pi}
 \end{aligned}$$

(R-L series circuit)

$$P_{av} = \frac{V_m I_m}{4\pi} \left[\cos \phi (2\pi) - \frac{\sin(2\pi - \phi)}{2} - 0 + \frac{\sin(2\pi - \phi)}{2} \right]$$


$$P_{av} = \frac{V_m I_m}{4\pi} \left[\cos \phi (2\pi) + \frac{\sin \phi}{2} - \frac{\sin \phi}{2} \right]$$

$$P_{av} = \frac{V_m I_m}{4\pi} \cdot 2\pi \cdot \cos \phi$$

$$P_{av} = \frac{V_m I_m}{2} \cos \phi = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$

$$\boxed{P_{av} = V_{rms} \cdot I_{rms} \cdot \cos \phi}$$

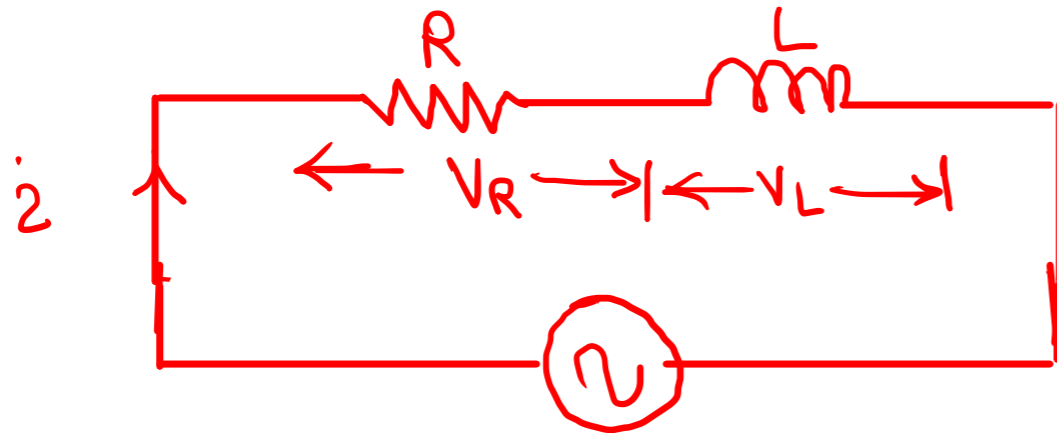Response of Resistor and Inductor series combination to ac input



$$V = V_m \sin(\omega t)$$

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} P_{inst} \cdot d\omega t$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \left[\frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m \sin 2\omega t}{2} \cos(2\omega t - \phi) \right] d\omega t$$

$$= \frac{1}{2\pi} \left[\frac{V_m I_m}{2} \cos \phi (\omega t) - \frac{V_m I_m}{2} \frac{\sin(2\omega t - \phi)}{2} \right]_0^{2\pi}$$

(R-L series circuit)

$$P_{av} = \frac{V_m I_m}{4\pi} \left[\cos \phi (2\pi) - \frac{\sin(2\pi - \phi)}{2} - 0 + \frac{\sin(0 - \phi)}{2} \right]$$


$$P_{av} = \frac{V_m I_m}{4\pi} \left[\cos \phi (2\pi) + \frac{\sin \phi}{2} - \frac{\sin \phi}{2} \right]$$

$$P_{av} = \frac{V_m I_m}{4\pi} \cdot 2\pi \cdot \cos \phi$$

$$P_{av} = \frac{V_m I_m}{2} \cos \phi = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$

$$P_{av} = V_{rms} \cdot I_{rms} \cdot \cos \phi$$

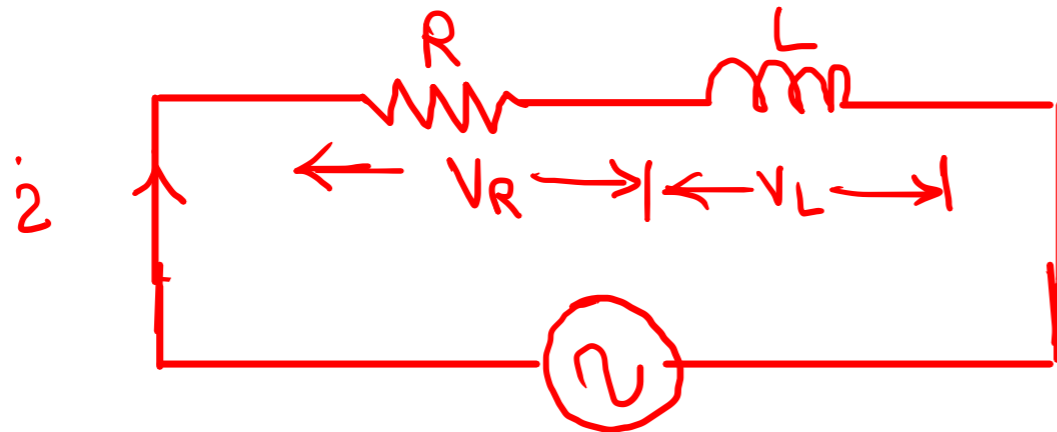Response of Resistor and Inductor series combination to ac input



$$V = V_m \sin(\omega t)$$

$$\begin{aligned}
 P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} P_{inst} \cdot d\omega t \\
 &= \frac{1}{2\pi} \int_0^{2\pi} \left[\frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m \sin 2\omega t}{2} \cos(2\omega t - \phi) \right] d\omega t \\
 &= \frac{1}{2\pi} \left[\frac{V_m I_m}{2} \cos \phi (\omega t) - \frac{V_m I_m}{2} \frac{\sin(2\omega t - \phi)}{2} \right]_0^{2\pi}
 \end{aligned}$$

(R-L series circuit)

$$P_{av} = \frac{V_m I_m}{4\pi} \left[\cos \phi (2\pi) - \frac{\sin(2\pi - \phi)}{2} - 0 + \frac{\sin(0 - \phi)}{2} \right]$$


$$P_{av} = \frac{V_m I_m}{4\pi} \left[\cos \phi (2\pi) + \frac{\sin \phi}{2} - \frac{\sin \phi}{2} \right]$$

$$P_{av} = \frac{V_m I_m}{4\pi} \cdot 2\pi \cdot \cos \phi$$

$$P_{av} = \frac{V_m I_m}{2} \cos \phi = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$

$$\boxed{P_{av} = V_{rms} \cdot I_{rms} \cdot \cos \phi}$$

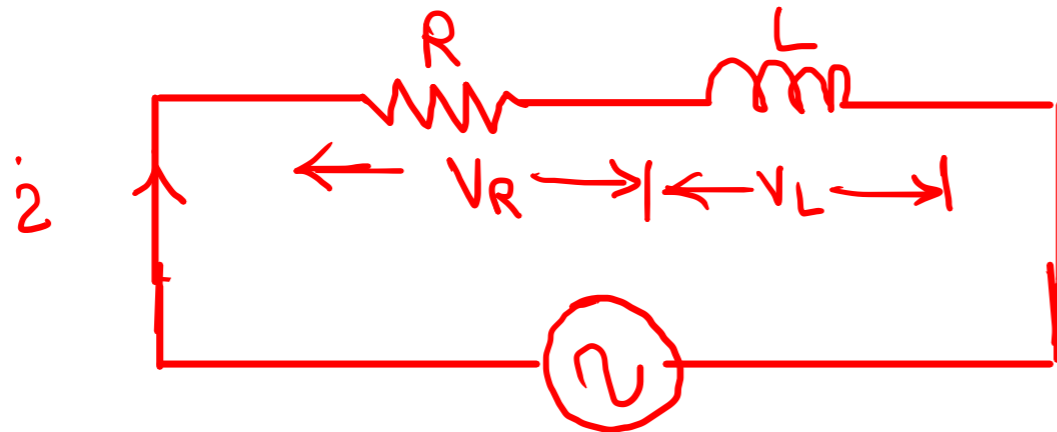Response of Resistor and Inductor series combination to ac input



$$V = V_m \sin(\omega t)$$

$$\begin{aligned}
 P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} P_{inst} \cdot d\omega t \\
 &= \frac{1}{2\pi} \int_0^{2\pi} \left[\frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m \sin 2\omega t}{2} \cos(2\omega t - \phi) \right] d\omega t \\
 &= \frac{1}{2\pi} \left[\frac{V_m I_m}{2} \cos \phi (\omega t) - \frac{V_m I_m}{2} \frac{\sin(2\omega t - \phi)}{2} \right]_0^{2\pi}
 \end{aligned}$$

(R-L series circuit)

$$P_{av} = \frac{V_m I_m}{4\pi} \left[\cos \phi (2\pi) - \frac{\sin(2\pi - \phi)}{2} - 0 + \frac{\sin(2\pi - \phi)}{2} \right]$$


$$P_{av} = \frac{V_m I_m}{4\pi} \left[\cos \phi (2\pi) + \frac{\sin \phi}{2} - \frac{\sin \phi}{2} \right]$$

$$P_{av} = \frac{V_m I_m}{4\pi} \cdot 2\pi \cdot \cos \phi$$

$$P_{av} = \frac{V_m I_m}{2} \cos \phi = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$

$$\boxed{P_{av} = V_{rms} \cdot I_{rms} \cdot \cos \phi}$$

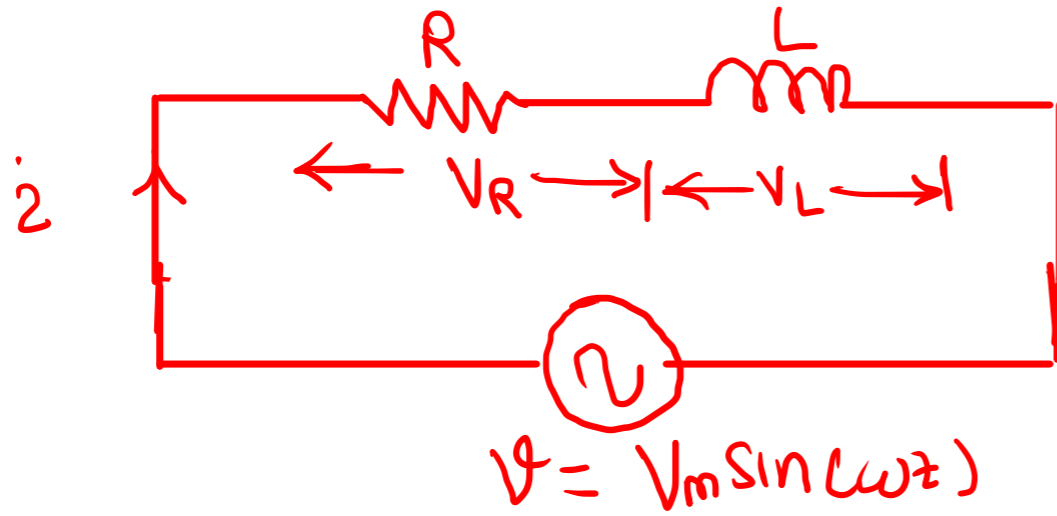Response of Resistor and Inductor series combination to ac input



^ R-L series circuit
⇒ Active power.


$$P_{av} = P_{active} = V_{rms} I_{rms} \cos \phi$$

→ ϕ is angle between voltage & current.



$\cos \phi$ ⇒ power factor.

$$P_{dc} = V \cdot I$$
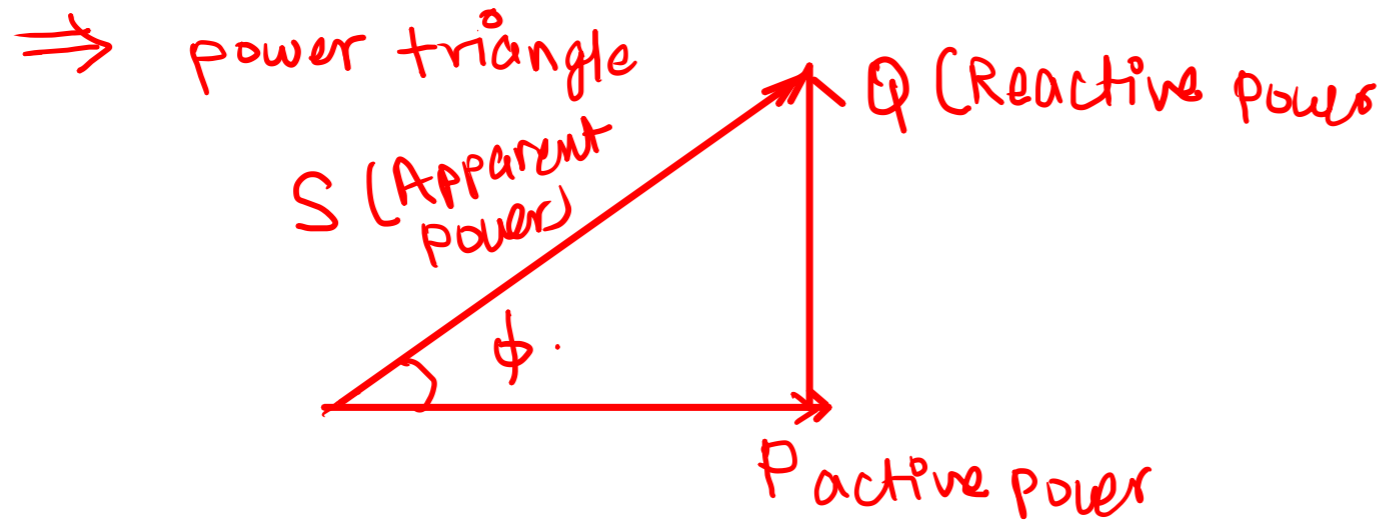
$$\rightarrow P_{ac} = V \cdot I \underline{\underline{\cos \phi}}$$



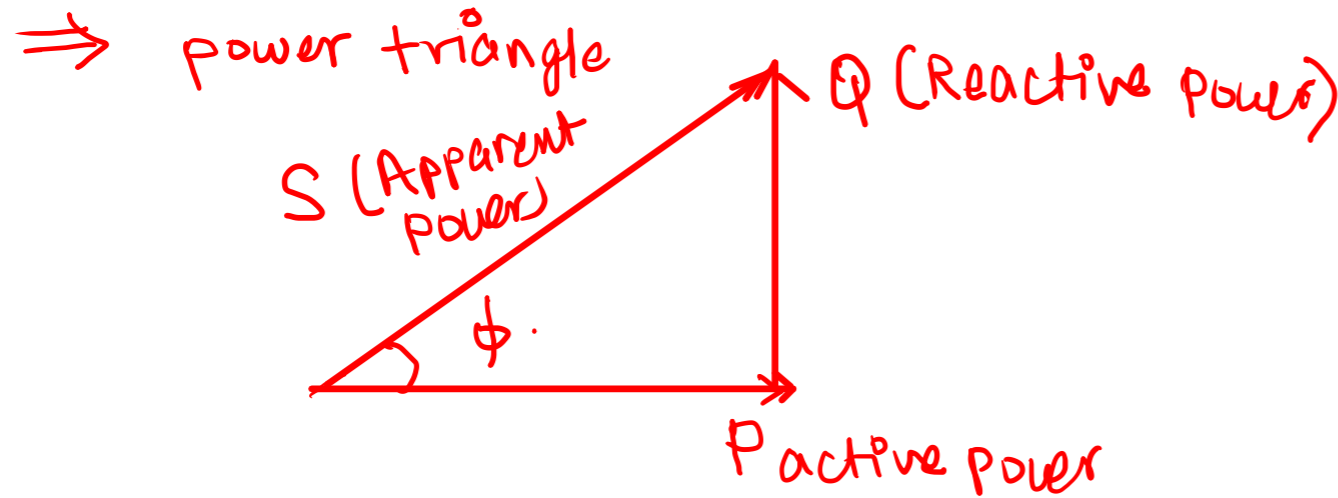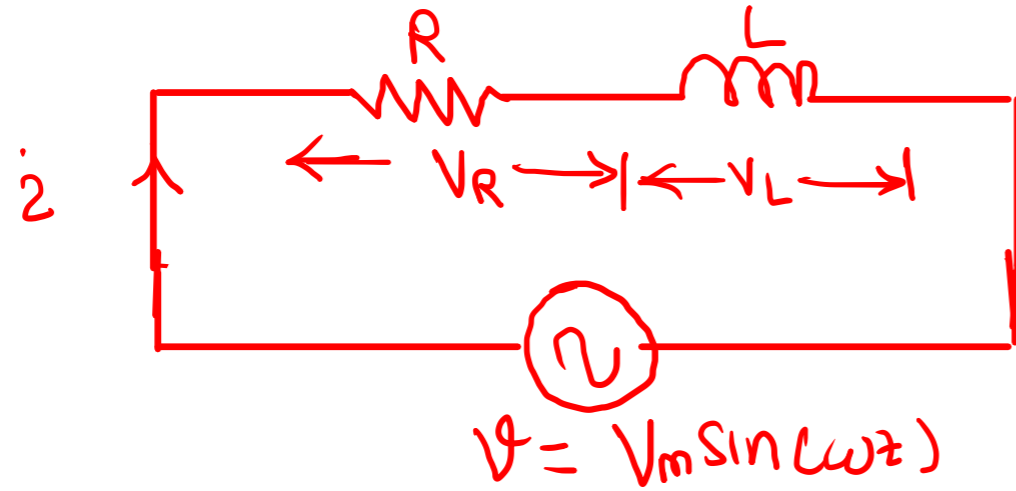
Response of Resistor and Inductor series combination to ac input




$$P_{\text{Active}} = V I \cos \phi \text{ (Watt)}$$

$$Q = V I \sin \phi \text{ (VAR)}$$

$$S = \sqrt{P^2 + Q^2} \text{ (VA)}$$

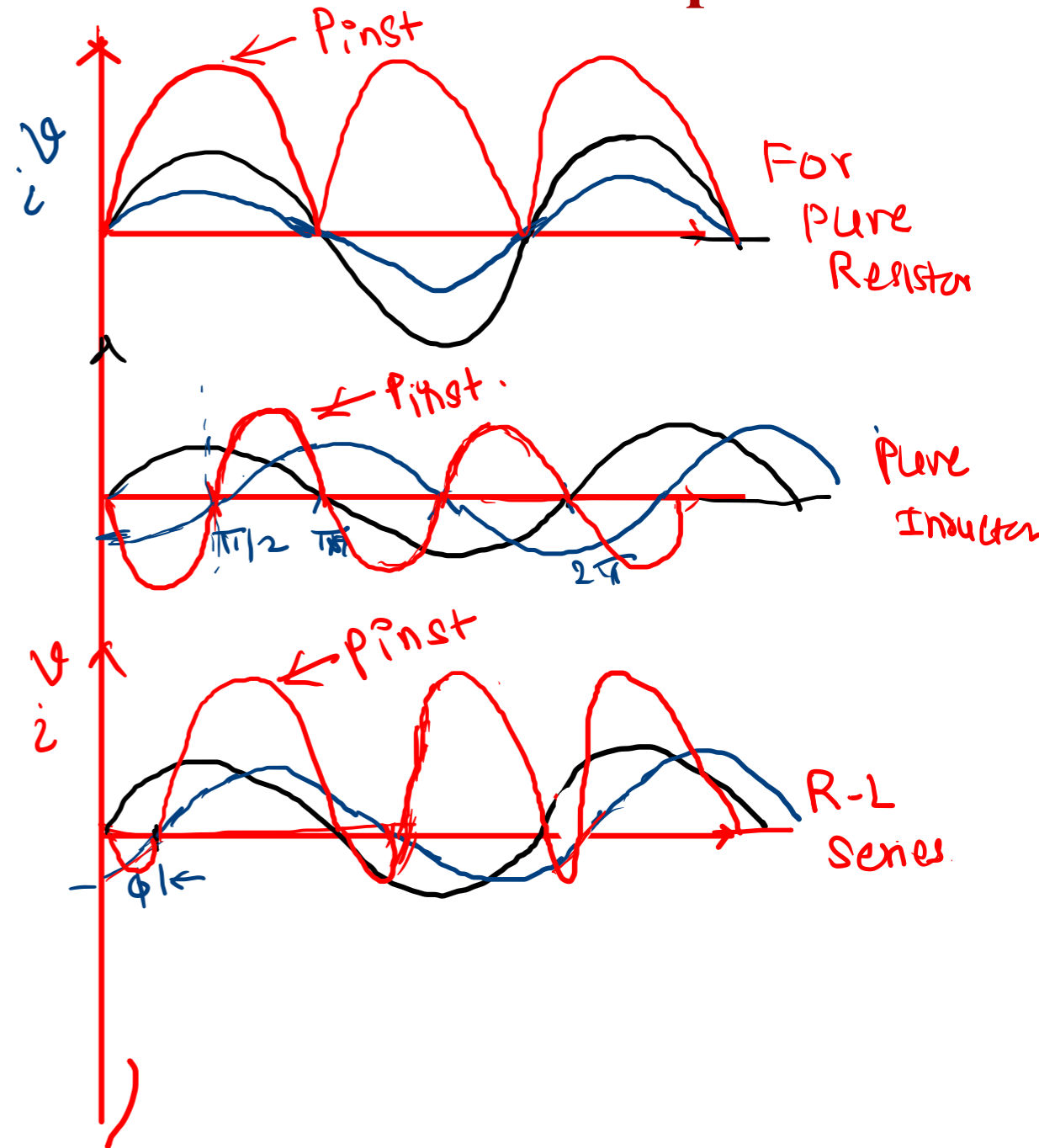

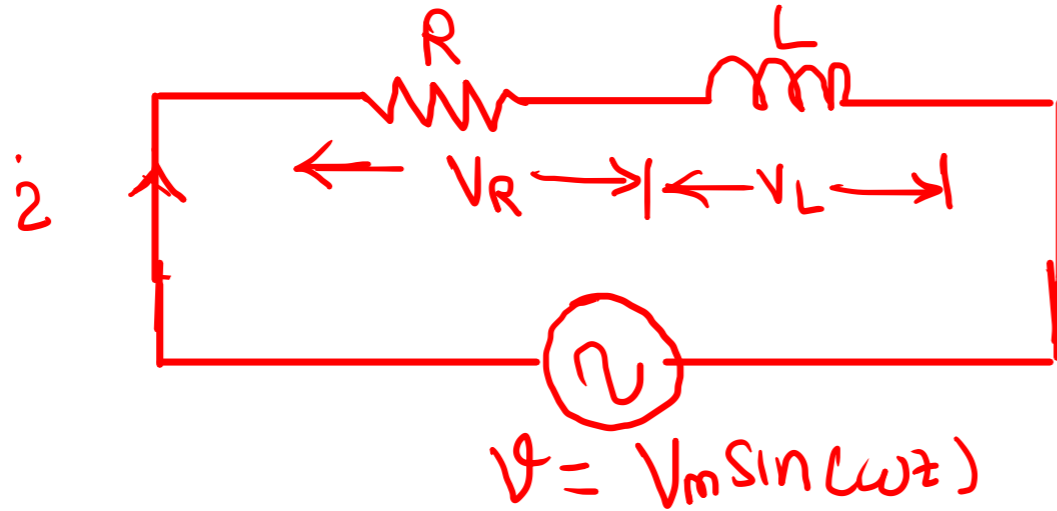Response of Resistor and Inductor series combination to ac input




$$\Rightarrow Z = R + jX_L$$

$$|Z| = \sqrt{R^2 + X_L^2}$$


$$\angle Z = \tan^{-1}\left(\frac{X_L}{R}\right) = \phi$$

$$PF = \cos \phi = \cos\left(\tan^{-1}\left(\frac{X_L}{R}\right)\right)$$

\Rightarrow Power factor $\cos \phi$.

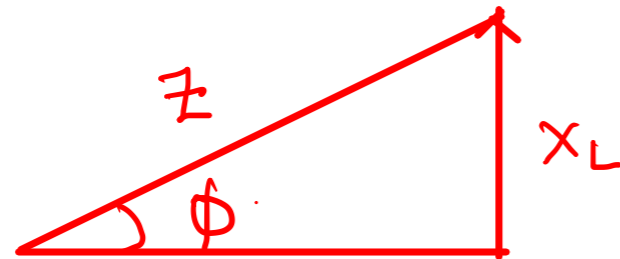


$$\cos \phi = \frac{R}{Z}$$

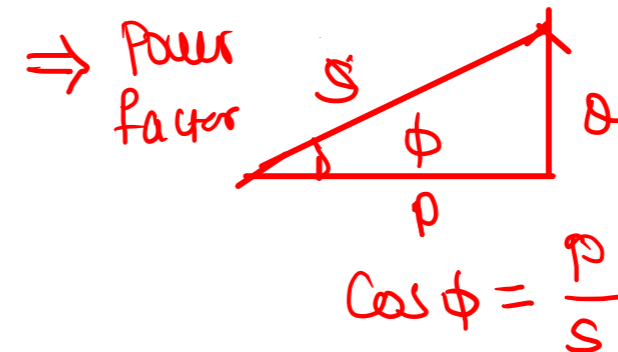


\Rightarrow Voltage triangle



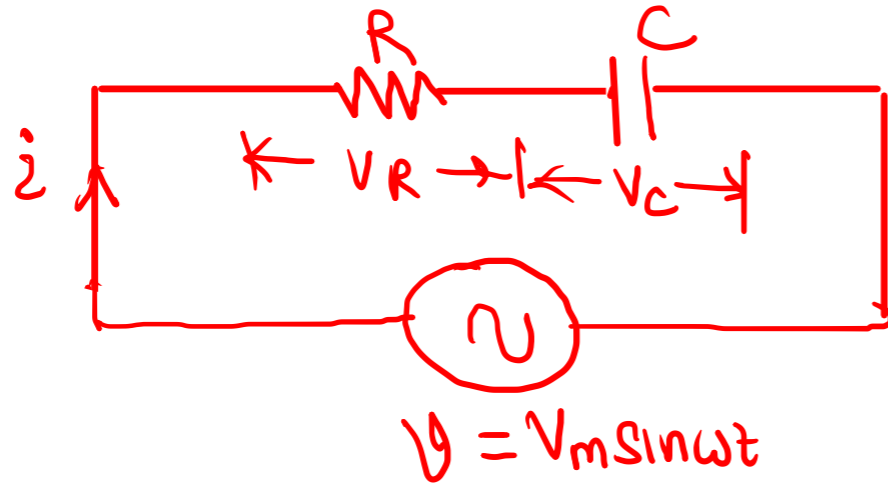Response of Resistor and capacitor series combination to ac input



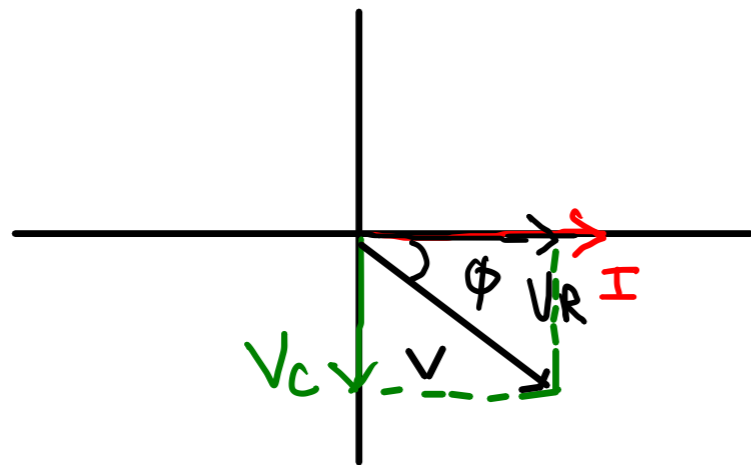⇒ phasor diagram. $\vec{V} = \vec{V}_R + \vec{V}_C$



Current I leads V by ϕ° .
Leading power factor

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + \phi)$$

$$P_{inst} = V_m \sin \omega t \cdot I_m \sin(\omega t + \phi)$$

$$P_{inst} = V_m I_m \sin(\omega t) \cdot \sin(\omega t + \phi)$$


$$P_{inst} = \frac{V_m I_m}{2} [\cos(\omega t - \omega t - \phi) - \cos(\omega t + \omega t + \phi)]$$

$$P_{inst} = \frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m}{2} \cos(2\omega t + \phi)$$


$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} P_{inst} \cdot d\omega t = \frac{V_m I_m}{2} \cos \phi$$

$$P_{av} = V_{rms} \cdot I_{rms} \cos \phi$$

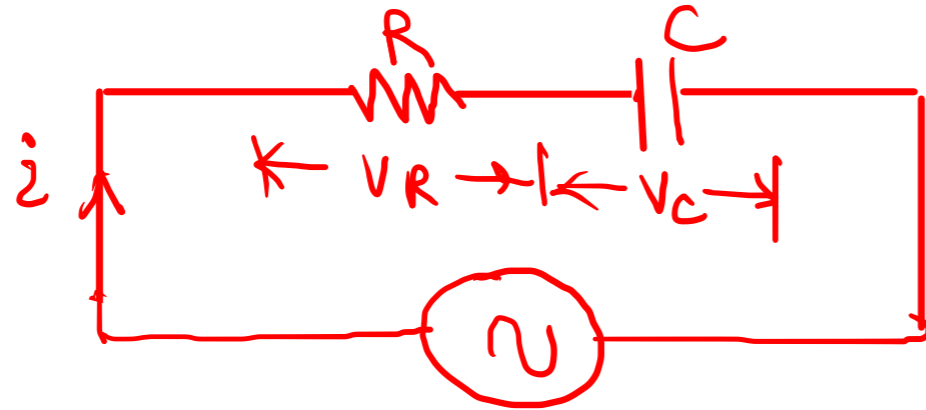Response of Resistor and capacitor series combination to ac input



$$v = V_m \sin \omega t$$

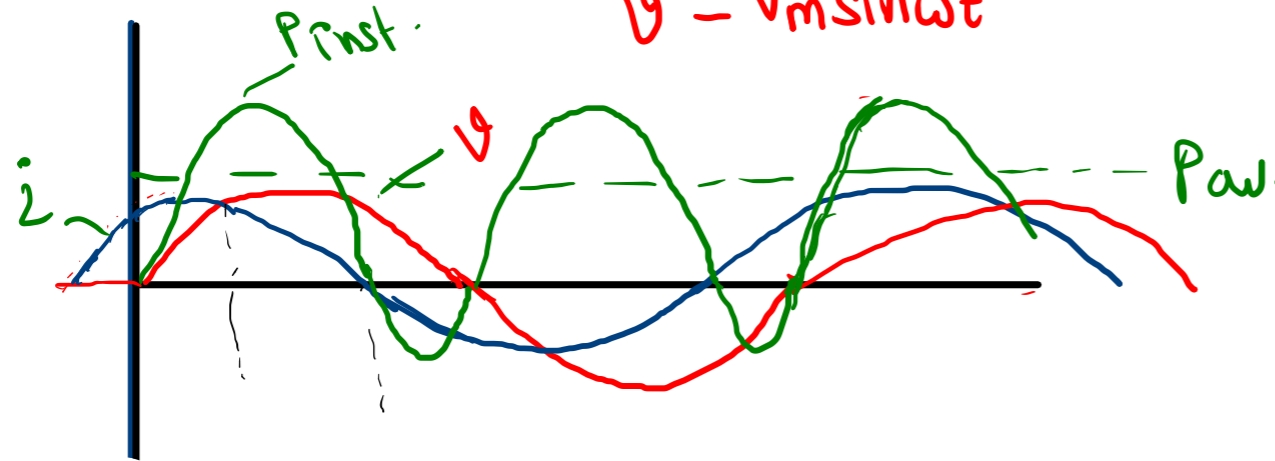


$$Z = R - jX_C$$

$$|Z| = \sqrt{R^2 + X_C^2}$$


$$\angle Z = \tan^{-1} \left(\frac{-X_C}{R} \right)$$

$\phi \rightarrow$ negative


\Rightarrow Voltage triangle

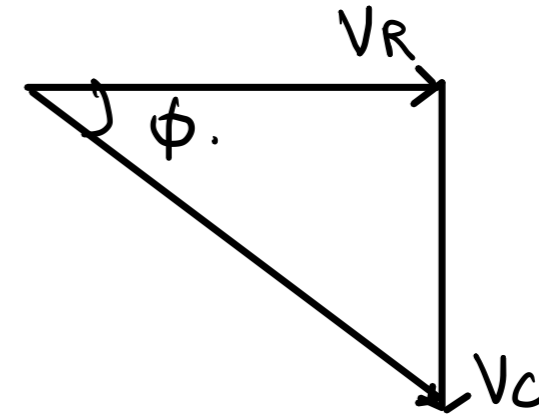


\Rightarrow Impedance triangle

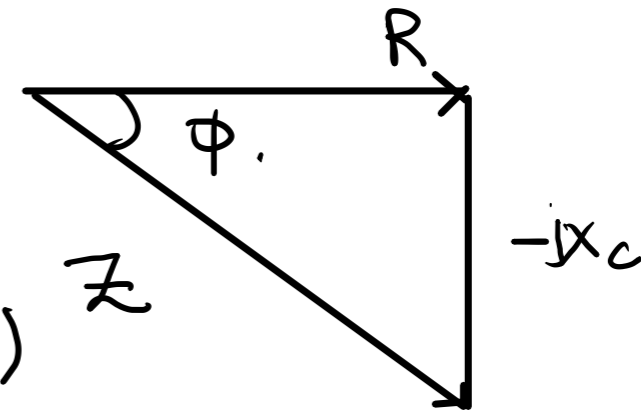

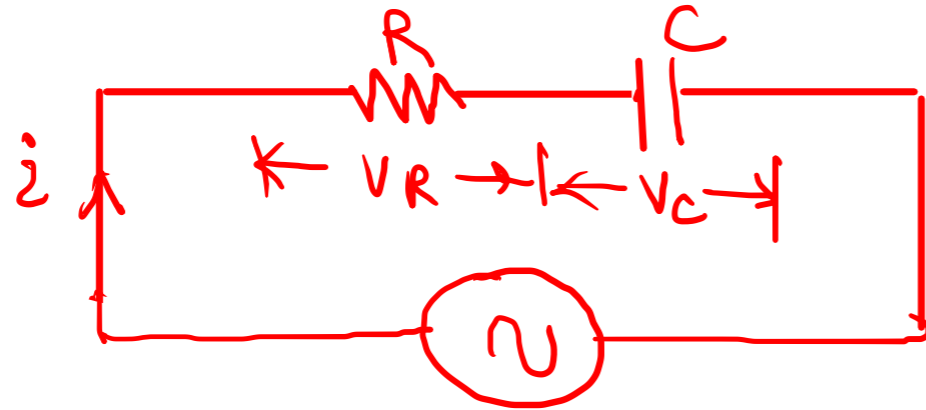Response of Resistor and capacitor series combination to ac input



$$v = V_m \sin \omega t$$

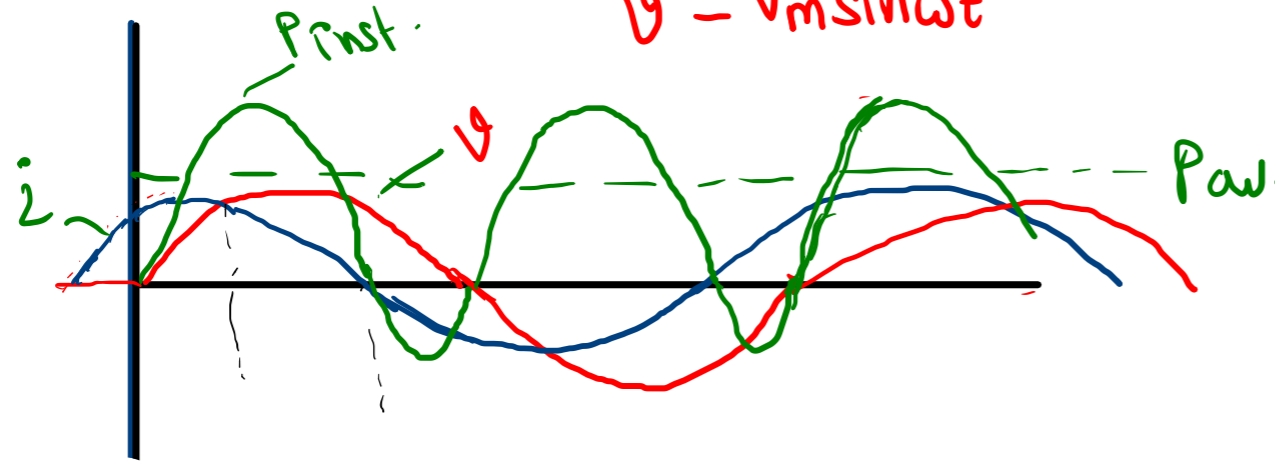


$$Z = R - jX_C$$

$$|Z| = \sqrt{R^2 + X_C^2}$$


$$\angle Z = \tan^{-1} \left(\frac{-X_C}{R} \right)$$

$\phi \rightarrow$ negative



\Rightarrow Voltage triangle

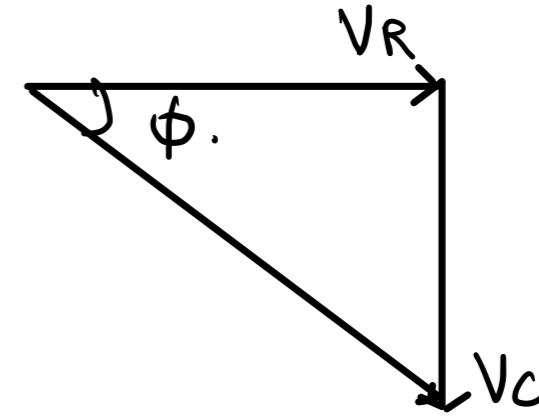

\Rightarrow Impedance triangle

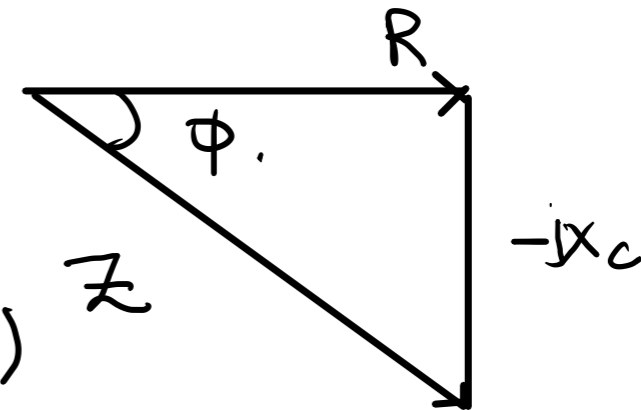


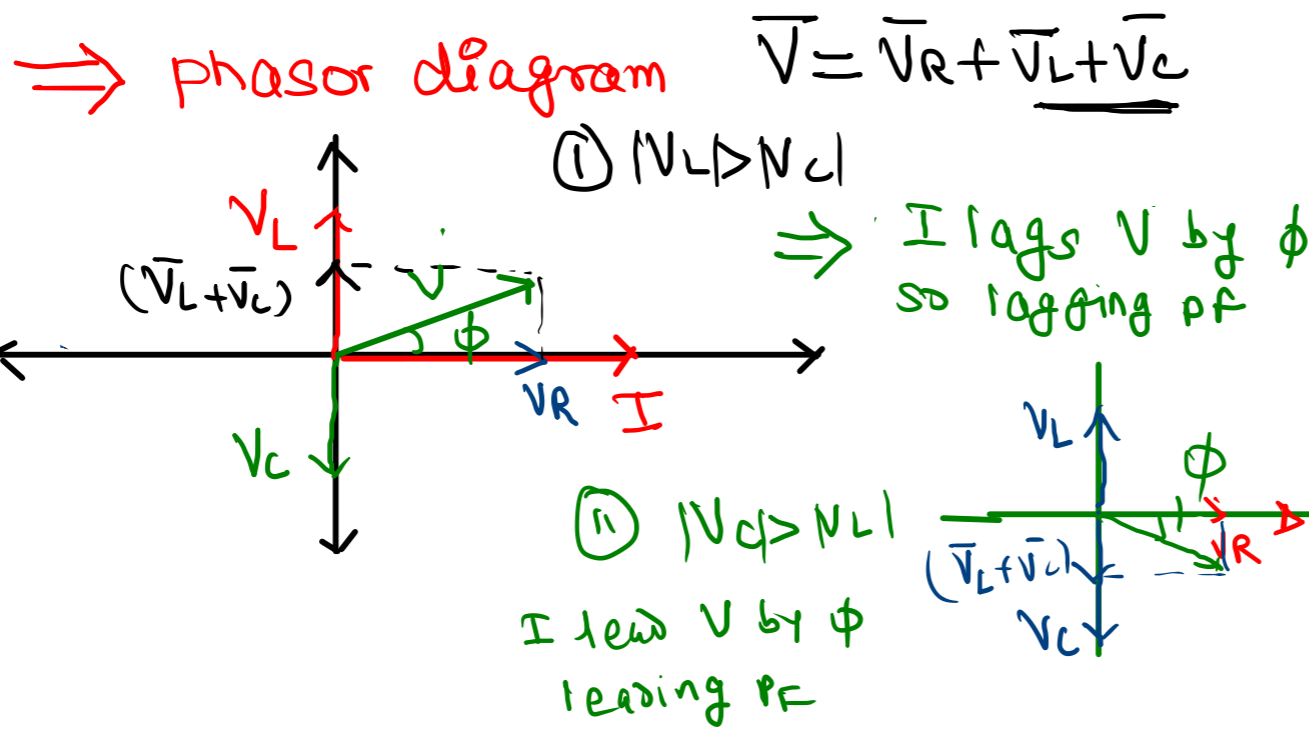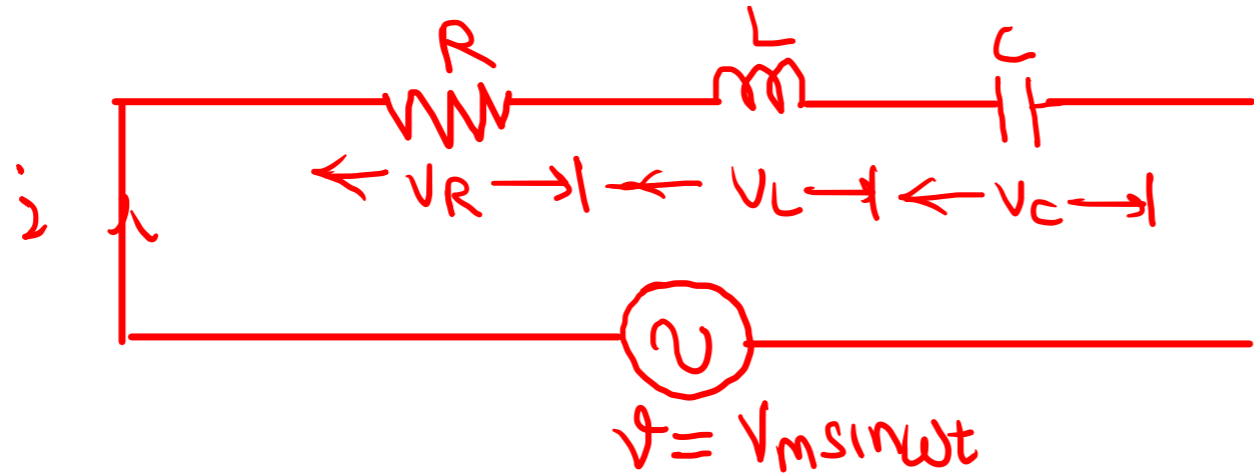Response of Resistor, inductor and capacitor series combination to ac input




⇒ $v = V_m \sin \omega t$
 $i = I_m \sin(\omega t \pm \phi)$

⇒ Impedance triangle

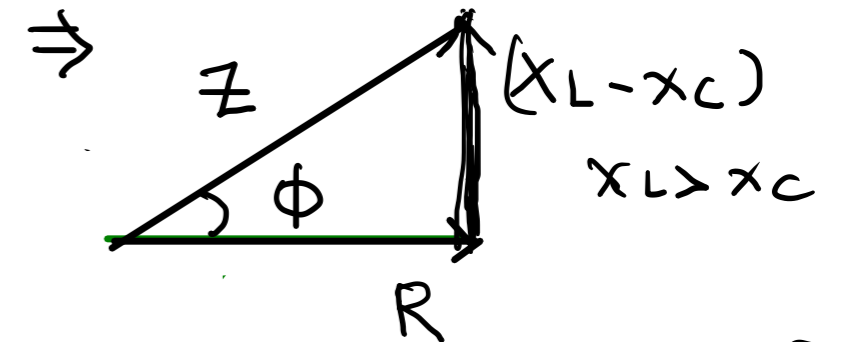


$Z = R + j(X_L - X_C) = R + jX$

⇒ $X_C > X_L$

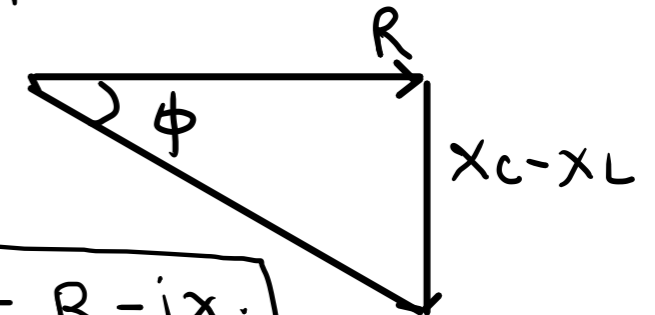

$Z = R - jX$

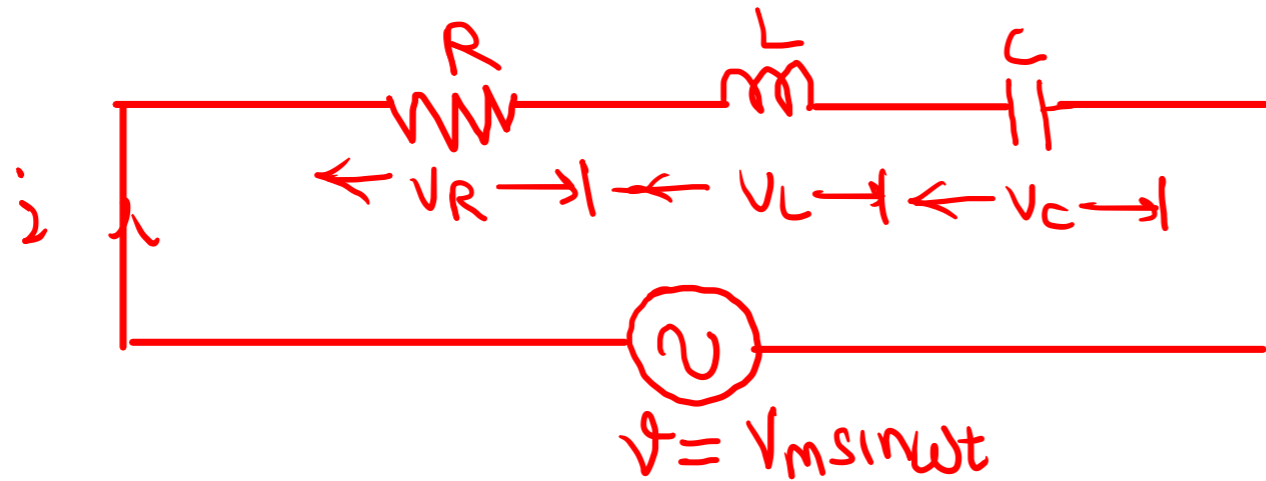
Response of Resistor, inductor and capacitor series combination to ac input



\Rightarrow if V & I known
 $f \rightarrow$ known
 $Z = \frac{V}{I}$

\Rightarrow

power triangle

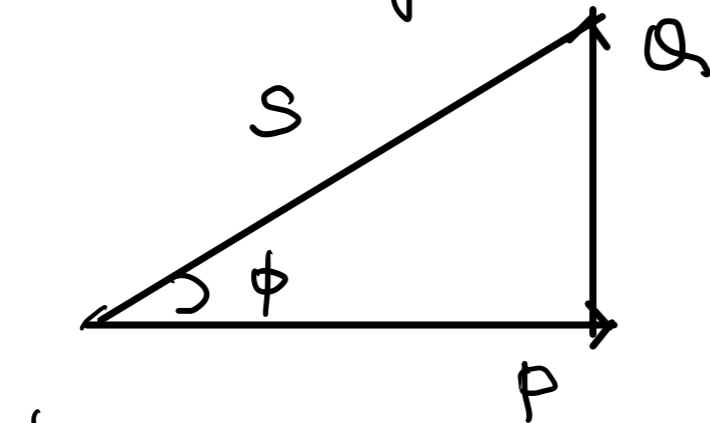

$\phi \angle$


$PF = \cos \phi$

\Rightarrow

R, L & C is known
 ω or f is known

$Z = R + j(X_L - X_C)$ ✓

$I = \frac{V}{Z}$ ✓

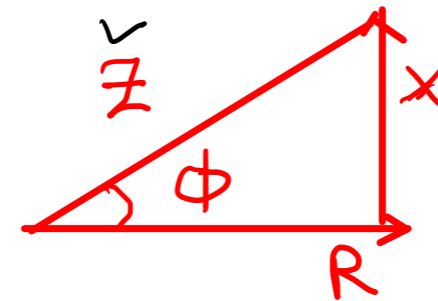


$\phi \angle$

$PF = \cos \phi$

$R = Z \cos \phi$ $X = Z \sin \phi$

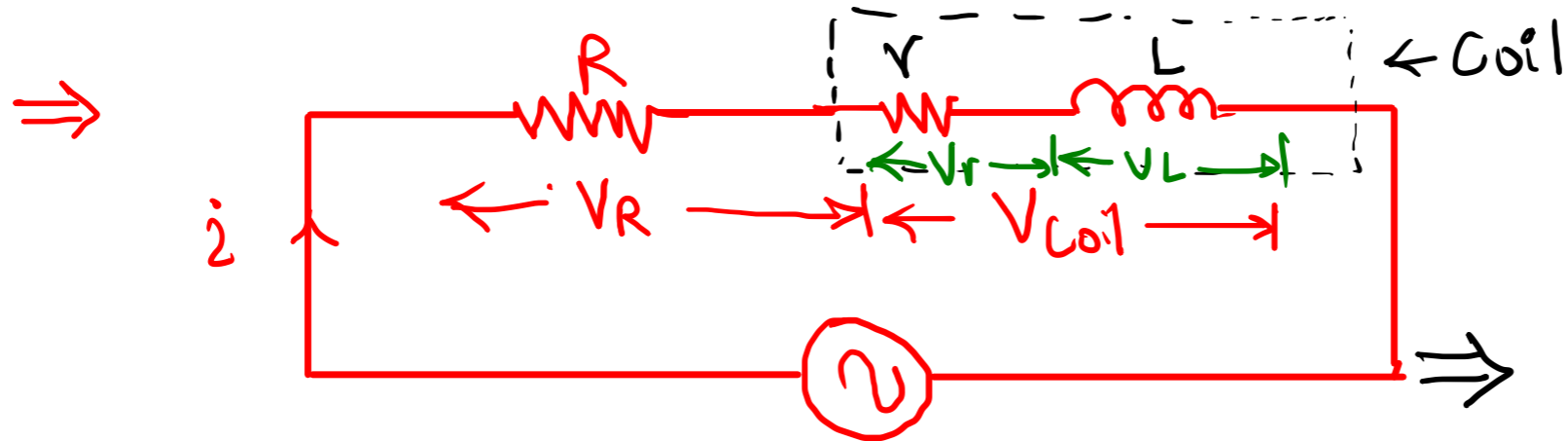R-L series circuit with AC input where inductor is Impure



ϕ_{coil} power factor angle of coil



ϕ overall pF angle of the circuit.

⇒ phasor diagram.

⇒ $\bar{V} = \bar{V}_R + \bar{V}_{coil}$
 $\bar{V}_{coil} = \bar{V}_r + \bar{V}_L$

$V = V_m \sin \omega t$

⇒ Volt age triangle

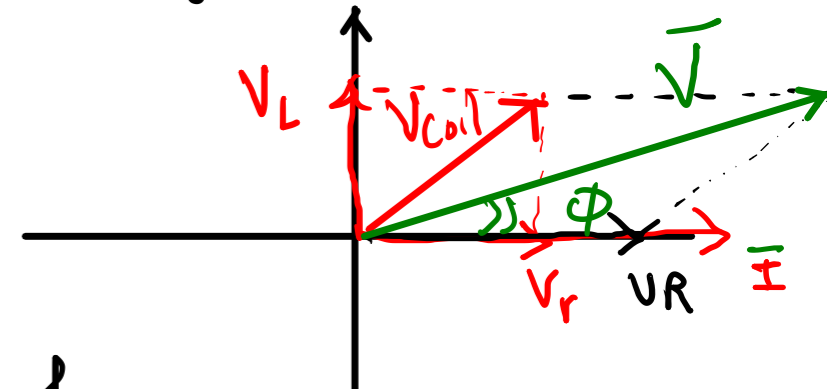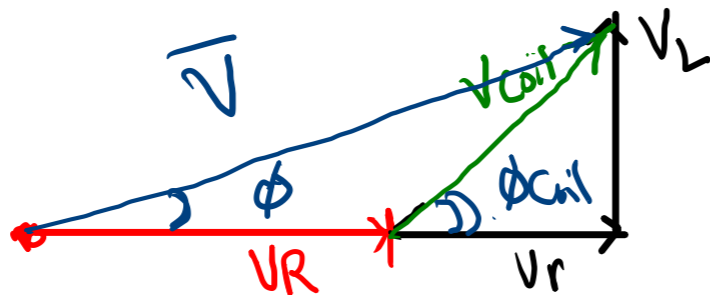


⇒ Law of parallelogram V_1, V_2, ϕ
 $\bar{V} = \bar{V}_1 + \bar{V}_2$

$$|\bar{V}| = \sqrt{V_1^2 + V_2^2 + 2 V_1 V_2 \cos \phi}$$

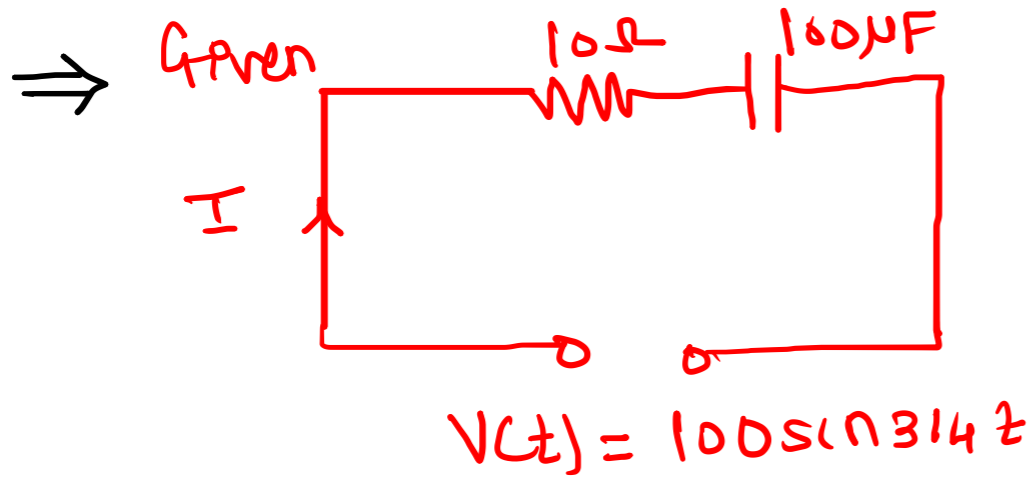
Example

① ⇒ A capacitor which has an internal resistance of 10Ω & capacitance value of $100\mu F$ is connected to ac voltage $V(t) = 100\sin(314t)$. Calculate current flowing through the circuit & construct voltage triangle.



$$I = \frac{V}{Z}$$

$$Z = R - jX_C$$

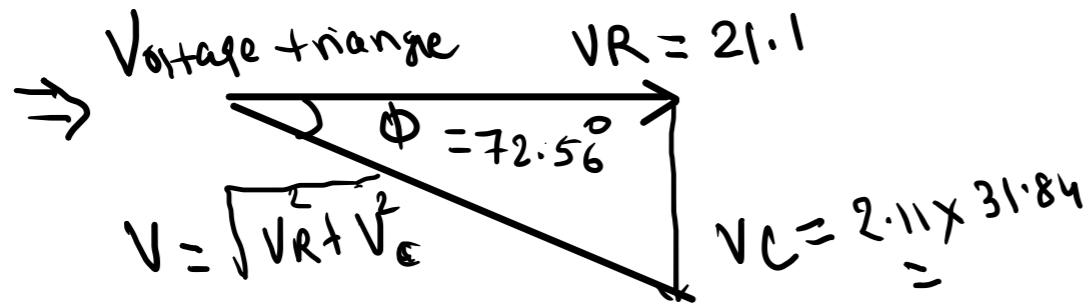

$$R = 10\Omega, C = 100\mu F, V(t) = V_m \sin(\omega t)$$

$$X_C = \frac{1}{\omega C}$$

$$\therefore \omega = 314$$

$$X_C = \frac{1}{314 \times 100 \times 10^{-6}} = 31.84\Omega$$


$$Z = (10 - j31.84) = \sqrt{10^2 + 31.84^2} \angle \tan^{-1}\left(\frac{-31.84}{10}\right)$$

$$I = \frac{100/\sqrt{2} \angle 0^\circ}{(10 - j31.84)} = \frac{70.71 \angle 0^\circ}{33.37 \angle -72.56^\circ}$$

$$I = 2.11 \angle 0 + 72.56^\circ = 2.11 \angle +72.56^\circ$$

$$I_m = 2.11 \times \sqrt{2} =$$

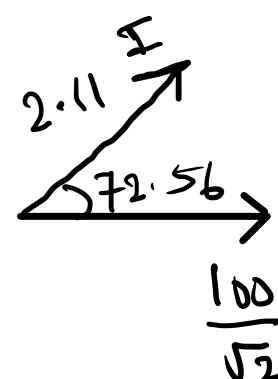
$$i = I_m \sin(\omega t + 72.56) = 2.98 \sin(314t + 72.56)$$



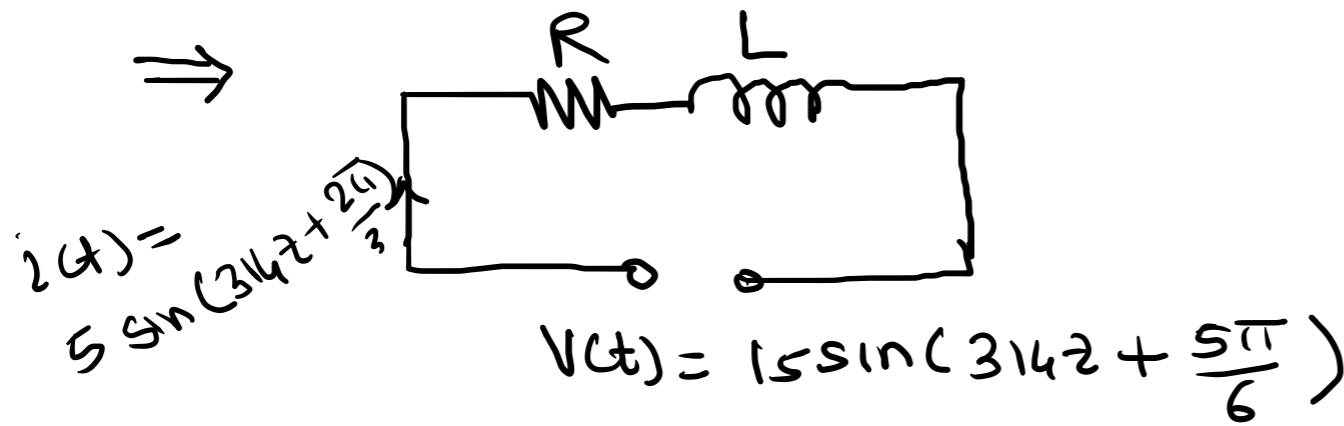Example ② In a series circuit containing a pure resistance and a pure inductor. The current & voltage are given as

$$i(t) = 5 \sin(314t + \frac{2\pi}{3}) \text{ \& } v(t) = 15 \sin(314t + \frac{5\pi}{6})$$

Find (i) Impedance of the circuit (ii) Value of resistance
(iii) Value of inductor (iv) Active Power (v) Power factor.



$$Z = \frac{V}{I} = \frac{15}{\frac{5}{\sqrt{2}}} \angle \frac{5\pi}{6} - \frac{2\pi}{3}$$

$$\frac{5}{\sqrt{2}} \angle \frac{2\pi}{3}$$

$$Z = 3 \angle 150 - 120^\circ$$

$$Z = R + jX_L$$

$$Z = 3 \angle 30^\circ$$

$$Z = 3 \cos 30^\circ + j 3 \sin 30^\circ$$

$$Z = 2.59 + j 1.5$$

$$\therefore R = 2.59 \Omega \quad X_L = 1.5 \Omega$$

$$X_L = \omega L \quad \therefore L = \frac{X_L}{\omega} = \frac{1.5}{314} = 4.78 \text{ mH}$$

$$\angle Z = \phi = \phi$$

$$= r \cos \phi + j r \sin \phi$$


$$\phi = 30^\circ$$

$$P = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos \phi$$

$$P = \frac{15}{\sqrt{2}} \times \frac{5}{\sqrt{2}} \cdot \cos 30^\circ = 37.5 \times \frac{\sqrt{3}}{2} = 32.47 \text{ Watts}$$

$$\text{PF} = \cos \phi = 0.86 \text{ (lagging)}$$

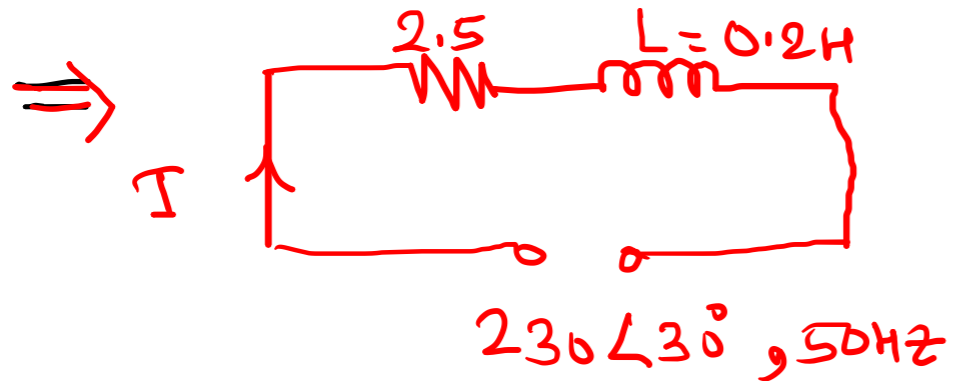3). A R-L series circuit is connected across $230\angle 30^\circ$, 50Hz supply. The value of R is 2.5 ohms and inductor $L=0.2$ H. Find current flowing through the circuit and power factor of the circuit.



$$\Rightarrow Z = R + jX_L$$

$$Z = 2.5 + j(2\pi fL)$$

$$Z = 2.5 + j(2\pi \times 50 \times 0.2)$$

$$Z = 2.5 + j62.8$$


$$Z = \sqrt{(2.5)^2 + (62.8)^2} \angle \tan^{-1}\left(\frac{62.8}{2.5}\right)$$

$$I = \frac{V}{Z} = \frac{230\angle 30^\circ}{62.85\angle 87.72^\circ}$$


$$I = \frac{230}{62.85} \angle (30^\circ - 87.72^\circ)$$

$$I = 3.65 \angle -57.72^\circ$$
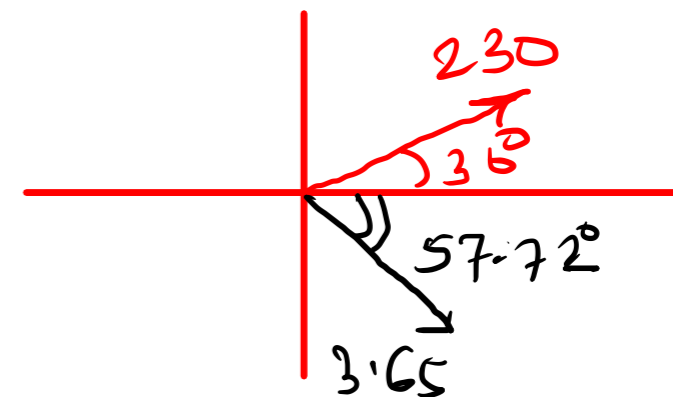
$$\text{PF} = \cos \phi = \cos (87.72^\circ) = 0.03 \text{ (lagging)}$$



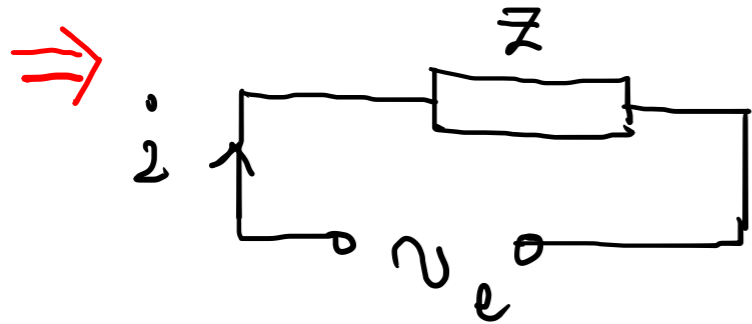4). Two elements series circuit is connected across ac source $e = 200\sqrt{2} \sin(314t + 20^\circ)$. The current flowing in the circuit is found to be $10\sqrt{2} \cos(314t - 25^\circ)$. Determine the parameters of the circuit.



$$e = 200\sqrt{2} \sin(314t + 20^\circ)$$

$$i = 10\sqrt{2} \cos(314t - 25^\circ)$$

$$i = 10\sqrt{2} \sin(314t - 25^\circ + 90^\circ)$$

$$i = 10\sqrt{2} \sin(314t + 65^\circ)$$


$$E = \frac{200\sqrt{2}}{\sqrt{2}} \angle 20^\circ$$

$$I = \frac{10\sqrt{2}}{\sqrt{2}} \angle 65^\circ$$

Since I leads E by $(65 - 20) = 45^\circ$

$$Z = \frac{E}{I} = \frac{200 \angle 20^\circ}{10 \angle 65^\circ}$$

$$Z = 20 \angle -45^\circ$$

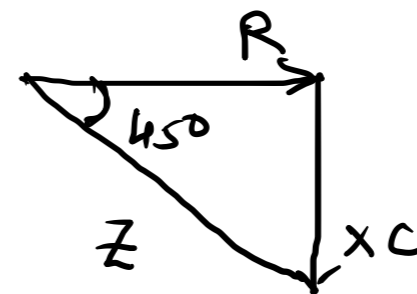

$$\cos 45^\circ = \frac{R}{Z}$$

$$R = Z \cos 45^\circ = 20 \cos(45^\circ)$$

$$X_c = Z \sin 45^\circ = 20 \sin(45^\circ)$$


$$X_c = \frac{1}{\omega C} = 14.14$$

$$\therefore C = \frac{1}{\omega \cdot X_c} = \frac{1}{314 \times 14.14}$$

$$C = 225 \times 10^{-6} = 225 \mu\text{F}$$

$$\underline{\underline{R = 14.14 \Omega}}$$

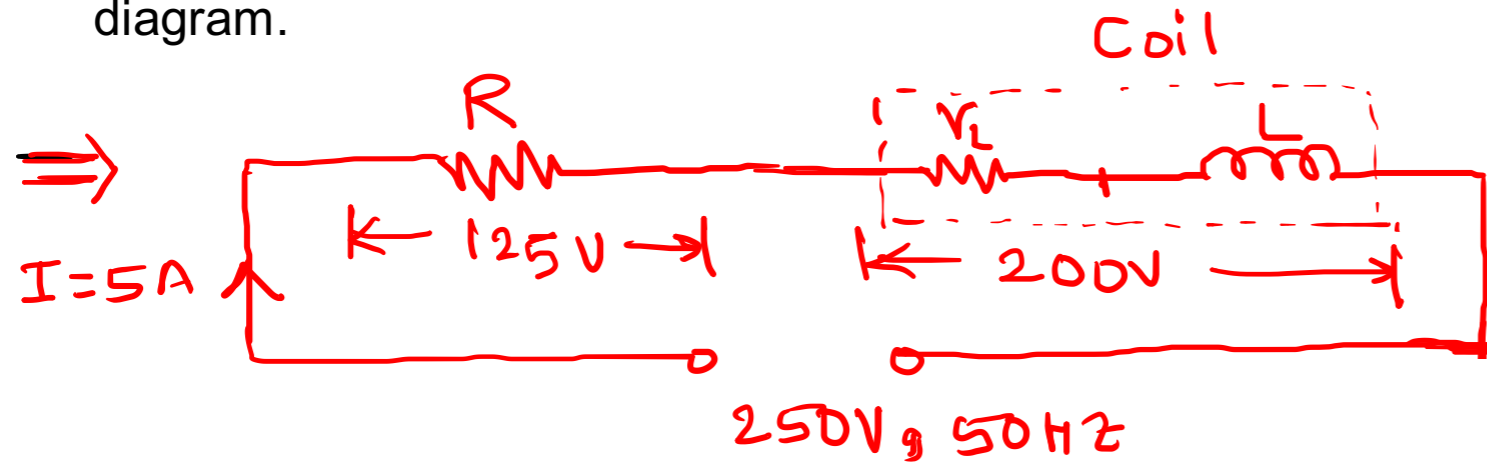5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V , 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.




$Z_{Coil} = ?$ $V_L = ?$
 $X_L = ?$ $P_{Coil} = ?$
 $P_{Total} = ?$

$\Rightarrow |Z_T| = \frac{250}{5} = 50 \Omega$

$R = \frac{125}{5} = 25 \Omega$

$|Z_{Coil}| = \frac{200}{5} = 40 \Omega$

\Rightarrow voltage triangle.

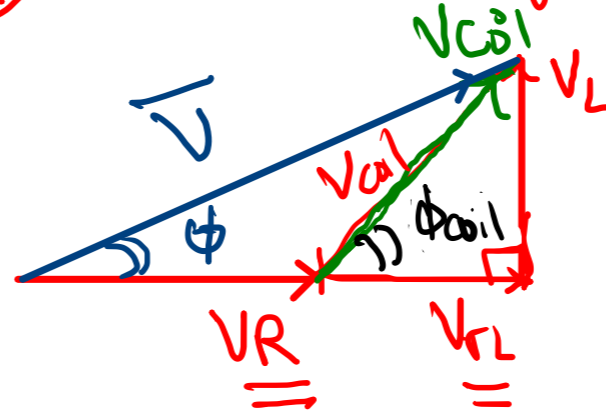

$\bar{V} = \bar{V}_R + \bar{V}_{coil}$ ✓


$\bar{V}_{coil} = \bar{V}_R + \bar{V}_L$ ✓

$V^2 = (V_R + V_{RL})^2 + (V_L)^2$


$V^2 = V_R^2 + 2V_R V_{RL} + V_{RL}^2 + V_L^2$

$V^2 = V_R^2 + 2V_R V_L + V_{Coil}^2$

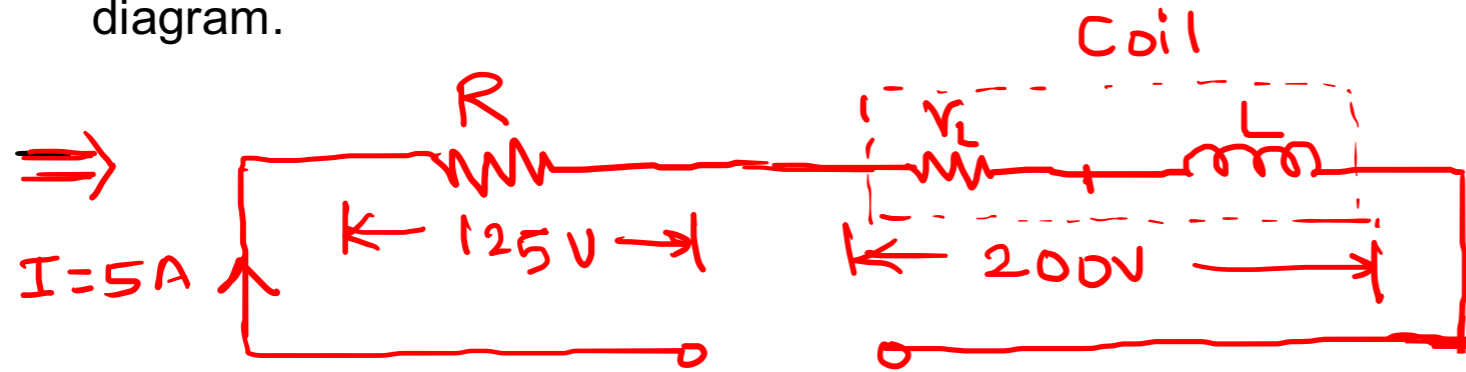5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V , 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.



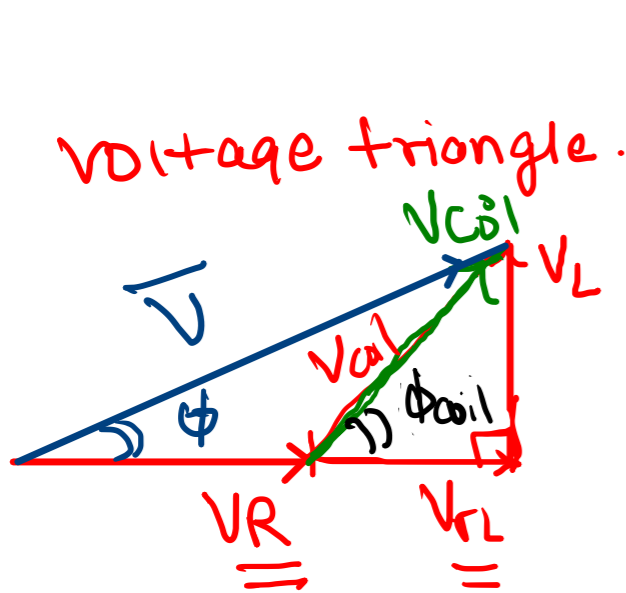$Z_{coil} = ?$ $V_L = ?$
 $X_L = ?$ $P_{coil} = ?$
 $P_{total} = ?$



250V, 50Hz

$$\bar{V} = \bar{V}_R + \bar{V}_{coil} \quad \checkmark$$

$$\bar{V}_{coil} = \bar{V}_{rL} + \bar{V}_L \quad \checkmark$$

$$V^2 = (V_R + V_{rL})^2 + (V_L)^2$$

$$V^2 = V_R^2 + 2V_R V_{rL} + \underline{V_{rL}^2} + \underline{V_L^2}$$

$$V^2 = V_R^2 + 2V_R V_{rL} + V_{coil}^2$$

$$(250)^2 = (125)^2 + 2 \cdot V_{rL} \cdot 125 + (200)^2$$

$$250 V_{rL} = (250)^2 - (125)^2 - (200)^2$$

$$250 V_{rL} = 6875$$


$$V_{rL} = 27.5V$$

$$r_L = \frac{V_{rL}}{I} = \frac{27.5}{5} = 5.5 \Omega$$

$$V_{coil}^2 = V_{rL}^2 + V_L^2$$

$$V_L^2 = V_{coil}^2 - V_{rL}^2 = (200)^2 - (27.5)^2$$

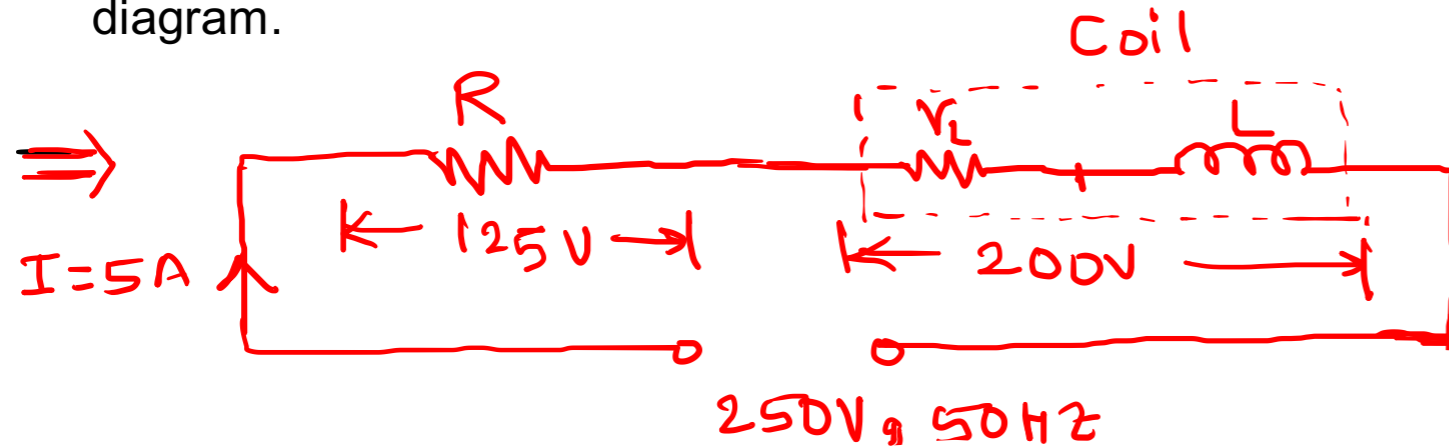5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V , 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.



$$Z_{\text{coil}} = ? \quad V_L = ?$$

$$X_L = ? \quad P_{\text{coil}} = ?$$

$$P_{\text{total}} = ?$$

$$r_L = \frac{V_{rL}}{I} = \frac{27.5}{5} = 5.5 \Omega$$

$$V_{\text{coil}}^2 = V_{rL}^2 + V_L^2$$

$$V_L^2 = V_{\text{coil}}^2 - V_{rL}^2 = (200)^2 - (27.5)^2$$

$$V_L = 198.1 \text{ V}$$

$$X_L = \frac{198.1}{5} = 39.63 \Omega$$

$$P_{\text{coil}} = I^2 r_L = (5)^2 \times 5.5 = 137.5 \text{ Watts}$$

$$\phi_{\omega} = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{39.63}{5.5} \right) = 82.098$$

$$P_{\text{coil}} = V \times I \cdot \cos \phi$$


$$P_{\text{coil}} = 200 \times 5 \times \cos(82.98) = 137.47 \text{ Watts}$$

The phasor diagram shows a right-angled triangle representing the coil's impedance. The hypotenuse is \$Z_{\text{coil}}\$, the adjacent side is \$R\$, and the angle between the hypotenuse and the adjacent side is \$\phi_{\omega}\$. The vertical side represents the inductive reactance \$X_L\$.

$$\cos \phi = \frac{R}{Z}$$


$$P_{\text{coil}} = V \times I \times \frac{R}{Z} = I \cdot Z \cdot I \cdot \frac{R}{Z} = I^2 R$$

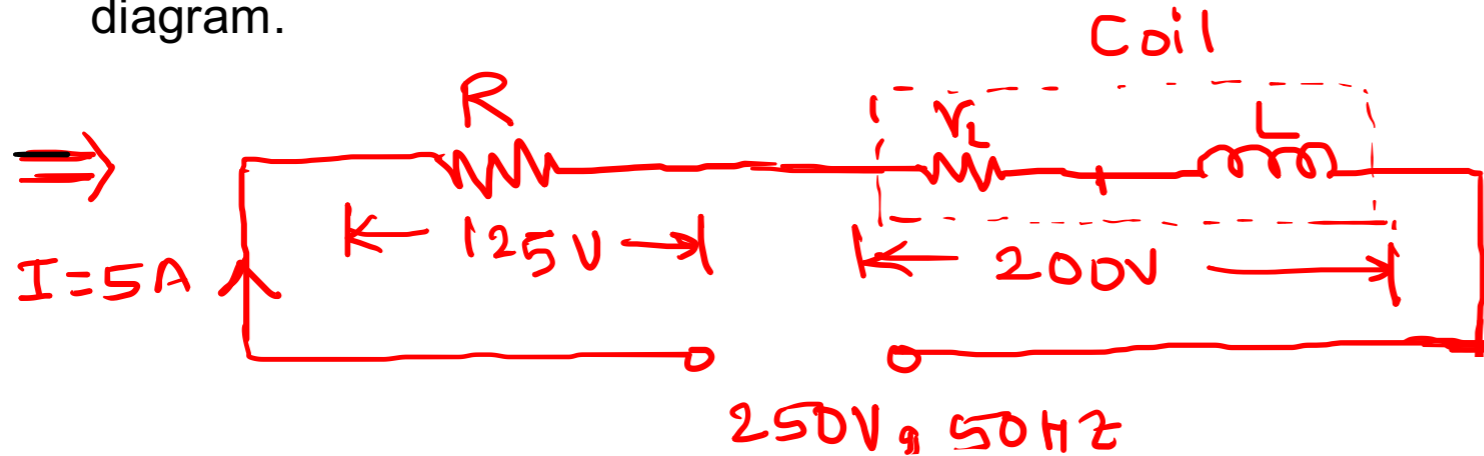5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V , 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.



$$\begin{aligned} Z_{\text{Coil}} &= ? & V_L &= ? \\ X_L &= ? & P_{\text{Coil}} &= ? \\ P_{\text{Total}} &= ? \end{aligned}$$

⇒ Phasor diagram.

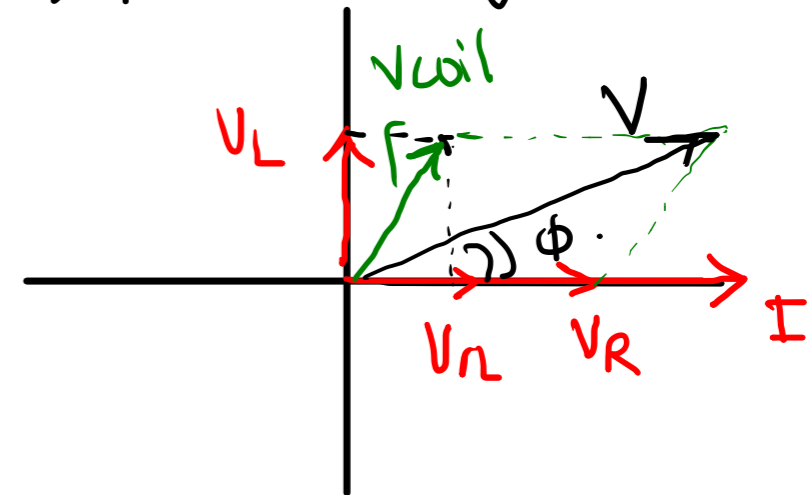

$$P_{\text{Total}} = I^2 (R + r_L) = (5^2) (25 + 5 \cdot 5) =$$

$$P_{\text{Total}} = 762.5 \text{ Watts}$$

$$P_{\text{Total}} = V \cdot I \cdot \cos \phi = 250 \times 5 \times \cos(52.4^\circ)$$

$$P_{\text{Total}} = 762.68 \text{ Watts.}$$

$$Z = (R + r_L) + j(X_L)$$


$$= (25 + 5 \cdot 5) + j(39.63)$$

$$Z = 30.5 + j39.63$$

$$\phi = \tan^{-1} \left(\frac{39.63}{30.5} \right)$$


$$\phi = 52.4^\circ$$

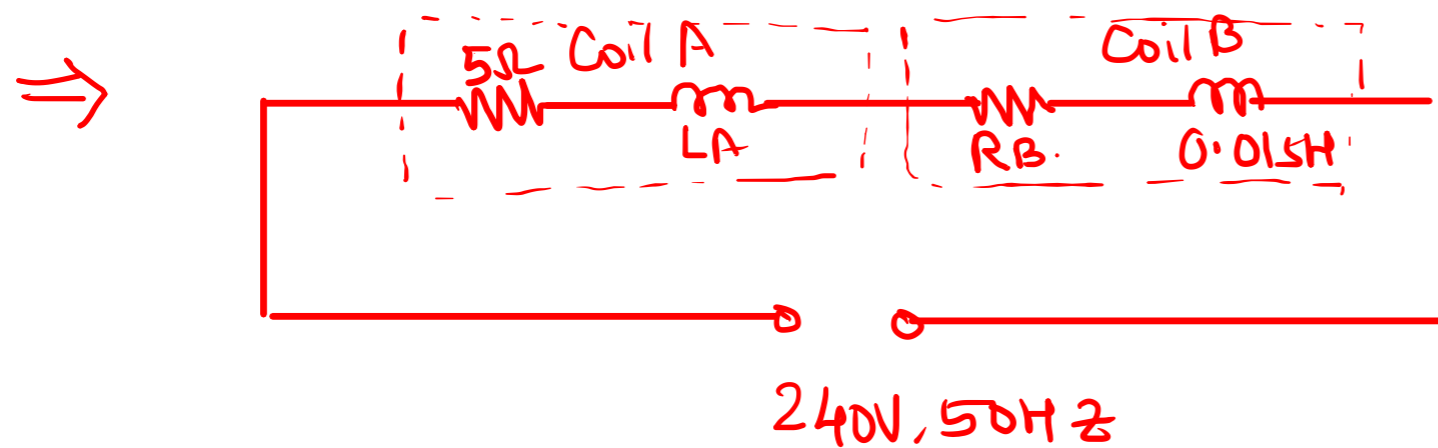6. Two coils A and B are connected in series across a 240 V, 50 Hz supply. The resistance of A is $5\ \Omega$ and inductance of B is 0.015 H. If the input from the supply is 3kWatts and 2kVAr. Find inductance of A and resistance of B. Calculate volatge across each coil.



$$L_A = ? \quad R_B = ?$$
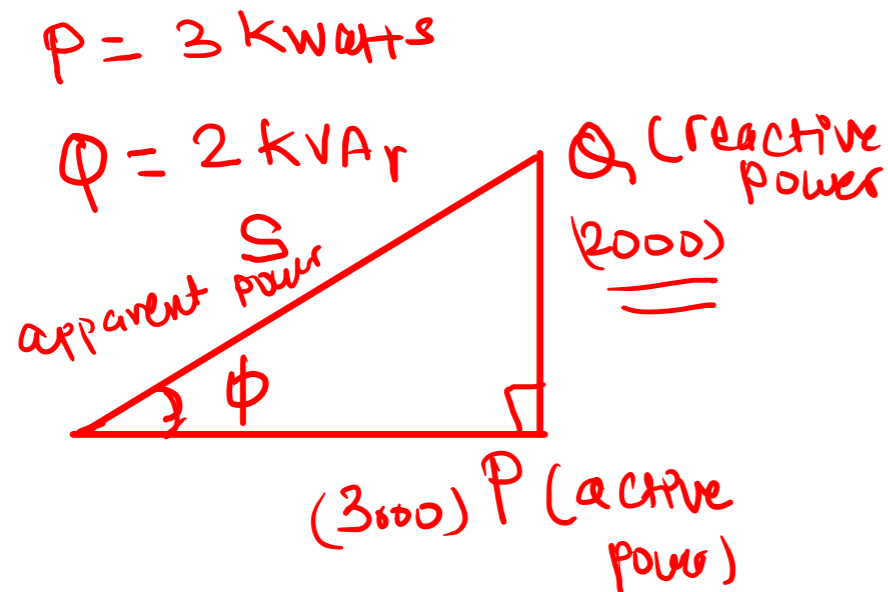
$$V_{\text{Coil A}} = ? \quad V_{\text{Coil B}} = ?$$



$$PF = \cos \phi = \frac{P}{S}$$

$$P^2 + Q^2 = S^2$$

$$S = \sqrt{(3000)^2 + (2000)^2}$$


$$S = 3605.5 \text{ VA}$$

$$S = V \times I$$

$$I = \frac{S}{V} = \frac{3605.5}{240} =$$


$$I = 15.02 \text{ A}$$
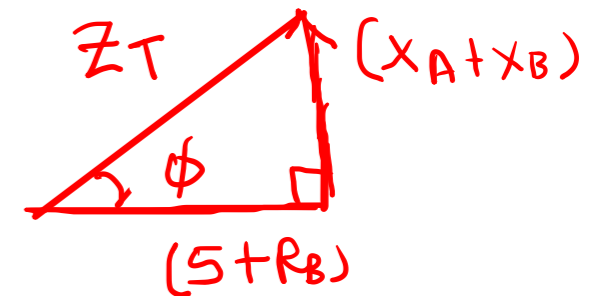
$$PF = \cos \phi = 0.83, \phi = 33.9^\circ$$



$$Z_T = \frac{V}{I} \angle \phi = \frac{240}{15.05} \angle 33.9^\circ$$

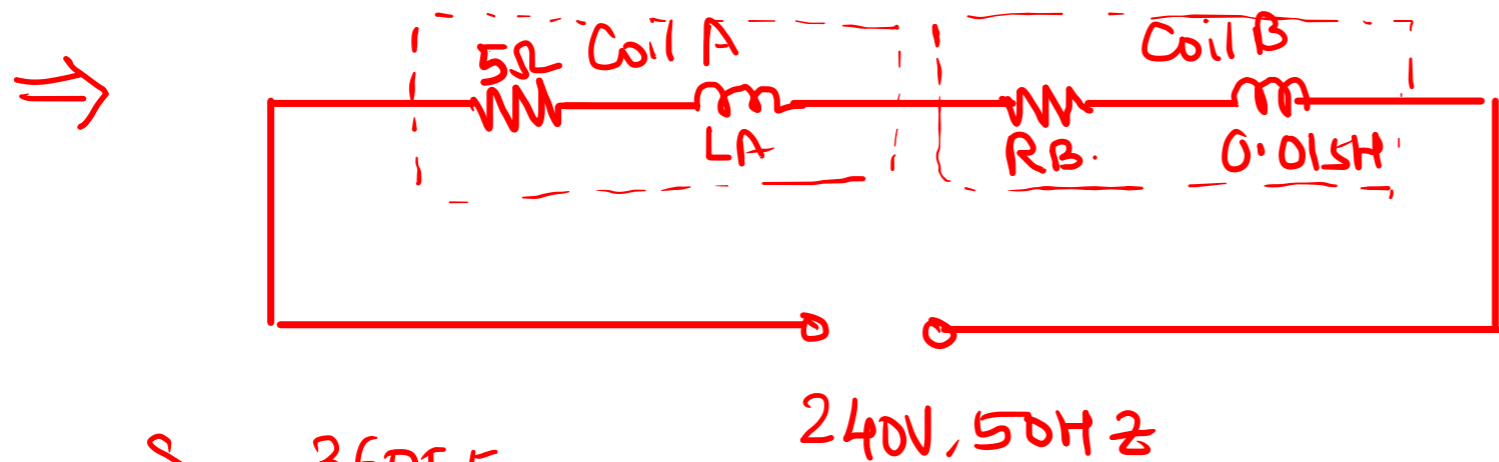6. Two coils A and B are connected in series across a 240 V, 50 Hz supply. The resistance of A is $5\ \Omega$ and inductance of B is 0.015 H. If the input from the supply is 3kWatts and 2kVAr. Find inductance of A and resistance of B. Calculate volatge across each coil.




$$L_A = ? \quad R_B = ?$$

$$V_{\text{Coil A}} = ? \quad V_{\text{Coil B}} = ?$$

$$I = \frac{S}{V} = \frac{3600 \cdot 5}{240} =$$

$$I = 15.02 \text{ A}$$
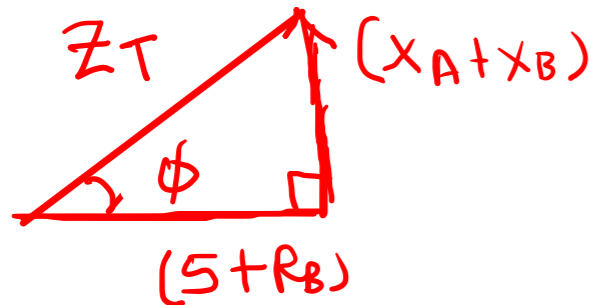
$$\text{PF} = \cos \phi = 0.83, \phi = 33.9^\circ$$



$$Z_T = \frac{V}{I} \angle \phi = \frac{240}{15.05} \angle 33.9^\circ$$

$$\cos \phi = \frac{5 + R_B}{Z_T}$$

$$0.83 \times \frac{240}{15.05} = 5 + R_B$$

$$R_B = 8.23 \ \Omega$$


$$\text{OR} \rightarrow P_{\text{act}} = I^2 (R_A + R_B)$$

$$3000 = (15.05)^2 \times (5 + R_B)$$

$$5 + R_B = \frac{3000}{(15.05)^2}$$

$$R_B = 8.26 \ \Omega$$

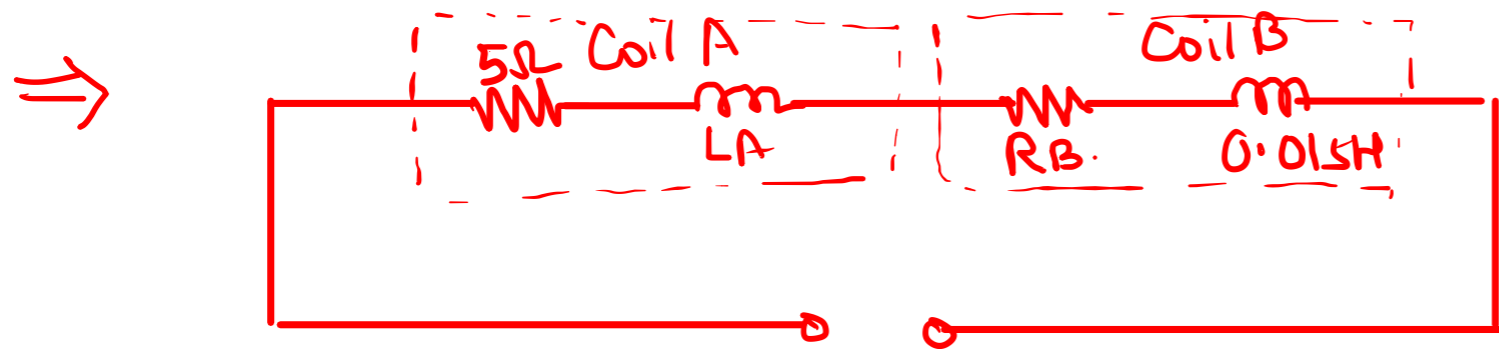6. Two coils A and B are connected in series across a 240 V, 50 Hz supply. The resistance of A is $5\ \Omega$ and inductance of B is 0.015 H. If the input from the supply is 3kWatts and 2kVAr. Find inductance of A and resistance of B. Calculate volatge across each coil.




$$L_A = ? \quad R_B = ?$$

$$V_{\text{Coil A}} = ? \quad V_{\text{Coil B}} = ?$$

$$I = \frac{S}{V} = \frac{3600 \cdot 5}{240} =$$

$$I = 15.02 \text{ A}$$
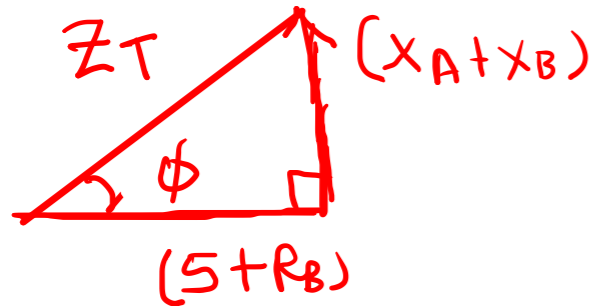
$$\text{PF} = \cos \phi = 0.83, \phi = 33.9^\circ$$



$$Z_T = \frac{V}{I} \angle \phi = \frac{240}{15.05} \angle 33.9^\circ$$

240V, 50Hz

$$\sin \phi = \frac{(X_A + X_B)}{Z_T}$$

$$X_B = 2\pi f \times 0.015$$

$$X_B = 2\pi \times 50 \times 0.015$$

$$X_B = 4.71 \Omega$$

$$X_A + X_B = \frac{240}{15.05} \sin(33.9)$$

$$X_A + X_B = 8.89 \Omega$$

$$X_A = 8.89 - 4.71$$


$$X_A = 4.18$$

$$2\pi f L_A = 4.18$$

$$L_A = \frac{4.18}{2\pi \cdot 50}$$

$$L_A = 13.3 \text{ mH}$$

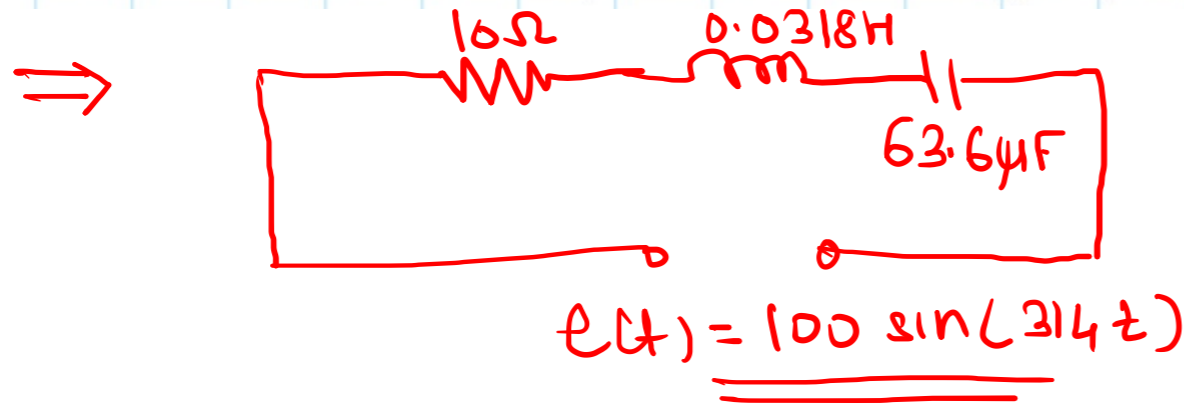7) A voltage $e(t) = 100 \sin(314t)$ is applied to a series circuit consisting of 10 ohm resistance, a 0.0318 H inductor and 63.6 μF capacitor. Calculate (i) expression for current (ii) Power factor (iii) Active power.



$i(t) = ?$
 $\text{PF} = \cos \phi = ?$
 $P_{\text{act}} = ?$

⇒ $E = \frac{100}{\sqrt{2}} \angle 0 \quad \omega = 314 \text{ rad/sec}$

$Z = 10 + j\left(\omega L - \frac{1}{\omega C}\right)$

$\omega L = 314 \times 0.0318 = 9.98 \Omega$

$\frac{1}{\omega C} = \frac{1}{314 \times 63.6 \times 10^{-6}} = 50.07 \Omega$

$Z = 10 + j(9.98 - 50.07)$

$Z = (10 - j40.09)$

$Z = 41.31 \angle -75.99^\circ$

$\text{PF} = \cos(-75.99^\circ) = 0.24 \text{ (leading)}$


$I = \frac{V}{Z} = \frac{70.7 \angle 0}{41.31 \angle -75.99} = 1.71 \angle 75.99$

$i(t) = 1.71 \times \sqrt{2} \sin(314t + 75.99^\circ)$

$P_{\text{act}} = V_{\text{rms}} \cdot I_{\text{rms}} \cos \phi$

$= \frac{100}{\sqrt{2}} \times 1.71 \times 0.24 = 29.01 \text{ Watts}$

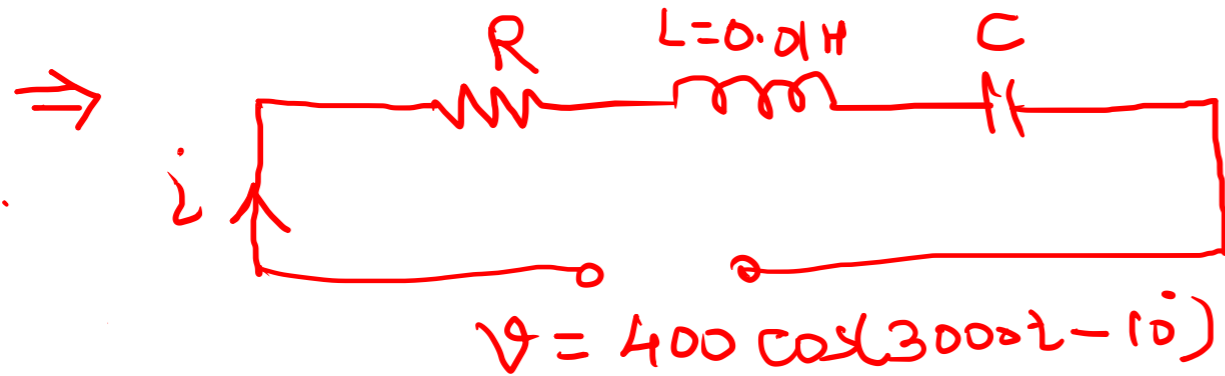8). A resistance R , an inductor $L=0.01$ H and a capacitance C are connected in series when voltage $v = 400 \cos(3000t - 10^\circ)$ is applied to a series combination. if the current is $i = 10\sqrt{2} \cos(3000t - 55^\circ)$. Find R and C .



$$i = 10\sqrt{2} \cos(3000t - 55^\circ), \quad \omega = 3000$$

$$v = 400 \sin(3000t - 10^\circ + 90^\circ)$$

$$\checkmark v = 400 \sin(3000t + 80^\circ)$$


$$i = 10\sqrt{2} \sin(3000t - 55^\circ + 90^\circ)$$

$$\checkmark i = 10\sqrt{2} \sin(3000t + 35^\circ)$$

$$R = ? \quad C = ?$$

rms values
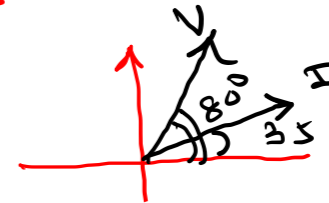
$$V = \frac{400}{\sqrt{2}} \angle 80^\circ, \quad I = \frac{10\sqrt{2}}{\sqrt{2}} \angle 35^\circ$$



$$Z = \frac{V}{I} = \frac{400/\sqrt{2} \angle 80^\circ}{10 \angle 35^\circ} = 28.3 \angle 45^\circ$$

$$Z = 20.01 + j20.01$$

$$\left. \begin{array}{l} \text{Components} \\ Z = R + jX \end{array} \right\} \begin{array}{l} \boxed{R = 20.01 \Omega} \\ \boxed{X_C = 9.99} \end{array}$$

$$X_L = \omega L = 3000 \times 0.01$$

$$X_L = 30 \Omega$$

$$X = X_L - X_C$$

$$X_C = 30 - 20.1$$

$$\boxed{X_C = 9.99}$$

$$X_C = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega \cdot X_C}$$

$$C = \frac{1}{3000 \times 9.99} = 33 \mu\text{F}$$

Concept Admittance (Y)

Admittance is Reciprocal of Impedance.

$$\bar{Y} = \frac{1}{Z} = \frac{1}{R \pm jX}$$

$$\bar{Y} = \frac{1}{R \pm jX} \times \frac{R \mp jX}{R \mp jX}$$

$$Y = \frac{R \mp jX}{R^2 + X^2}$$

$$Y = \frac{R}{R^2 + X^2} \mp j \frac{X}{R^2 + X^2}$$

$$Y = G \mp jB$$

Admittance = (\sim) (mho)
Siemens

Conductance (\sim)
(mho)
Siemens

Suceptance (\sim)
(mho)
Siemens

For R-L circuit


$$Z = \underline{R + jX_L} \text{ \& } Y = G - jB$$

for R-C circuit

$$Z = R - jX_C \text{ \& } Y = G + jB$$



R-L Parallel Circuit

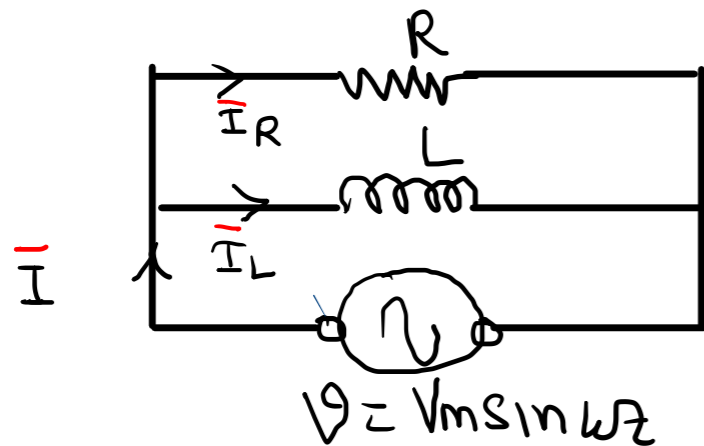


$$\vec{I} = \vec{I}_R + \vec{I}_L$$

⇒ Current is lagging voltage by an angle ϕ
So Lagging power factor



phasor diagram

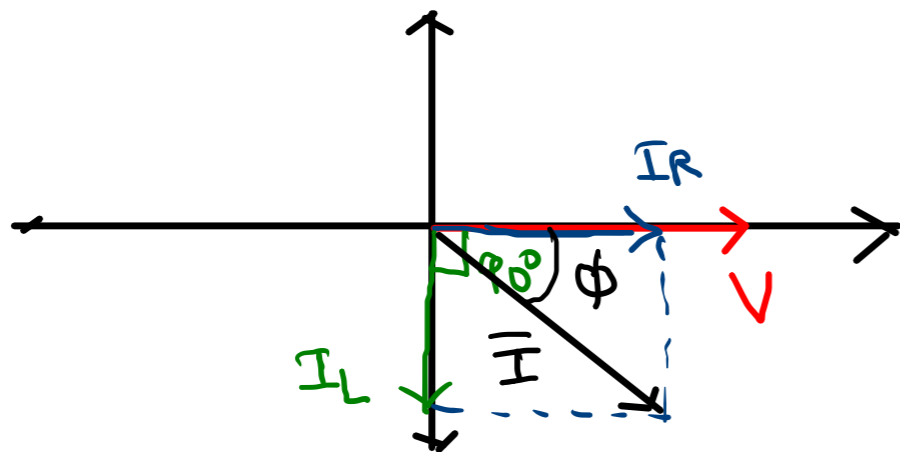

⇒ since R & L are in parallel
So equivalent impedance

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{jX_L}$$

Admittance $Y = G - j \frac{1}{X_L}$


$$\frac{V}{I} = Z = \frac{1}{Y}$$

$$P_{act} = V_{rms} I_{rms} \cos \phi$$

$$Q = V_m I_{rms} \sin \phi$$

$$S = V_{rms} \times I_{rms}$$

⇒ R-C Parallel Circuit

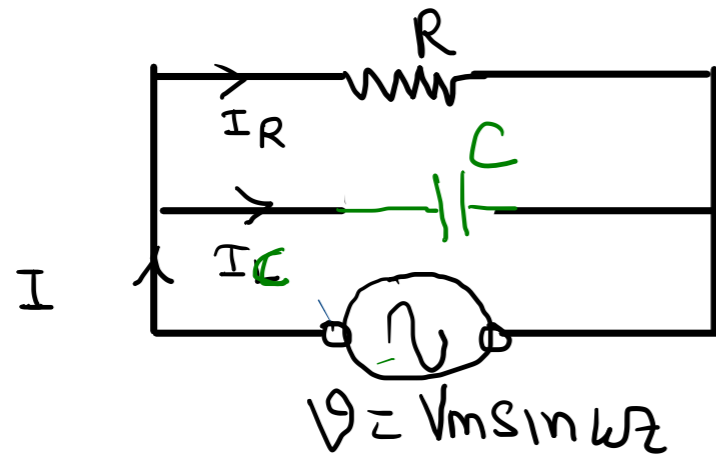


$$\bar{I} = \bar{I}_R + \bar{I}_C$$

Overall impedance of the circuit

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{-j(\frac{1}{\omega C})}$$

⇒ Phasor diagram.

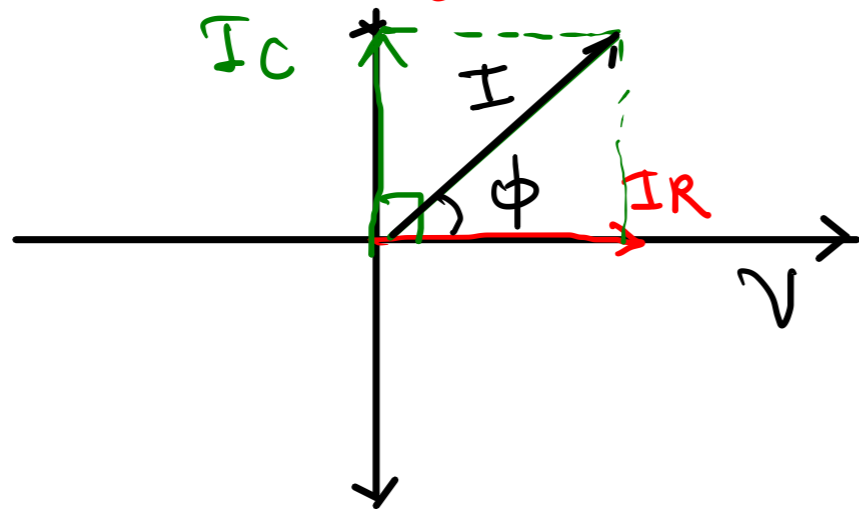


$$Y = G + j\omega C$$

Current is leading voltage by ϕ°


So PF = $\cos \phi$ (leading)

R-L-C Parallel Circuit

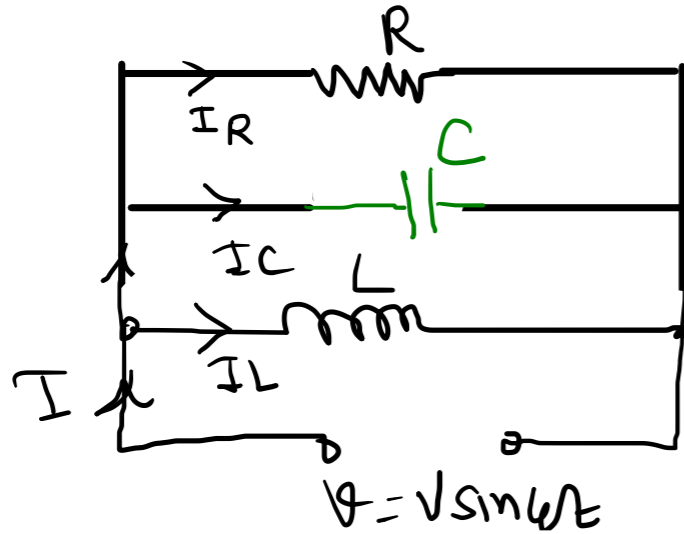


$$\bar{I} = \bar{I}_R + \bar{I}_L + \bar{I}_C$$


Case - (I) If $I_L > I_C$ ($X_L < X_C$)

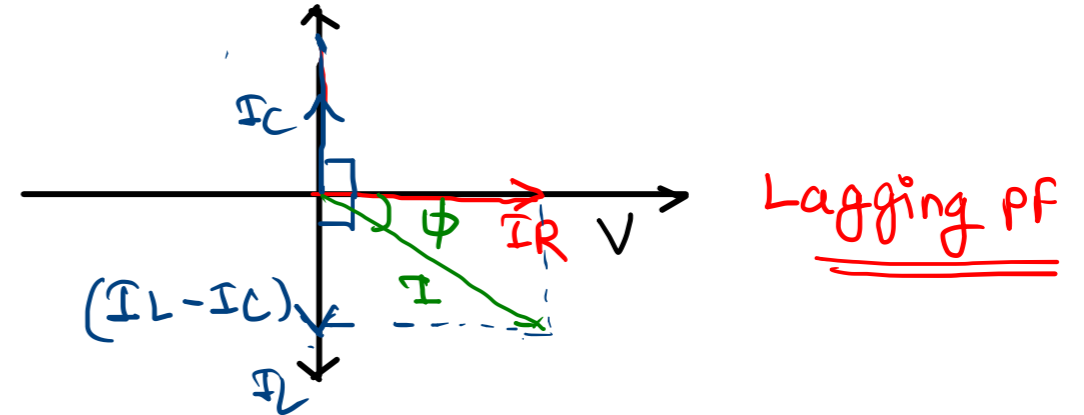


⇒ Phasor diagram.

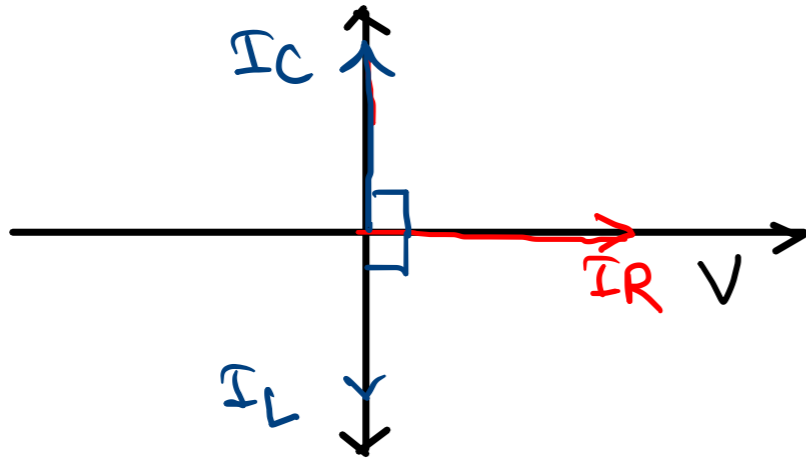

Case - (II) If $I_C > I_L$ ($X_C < X_L$)

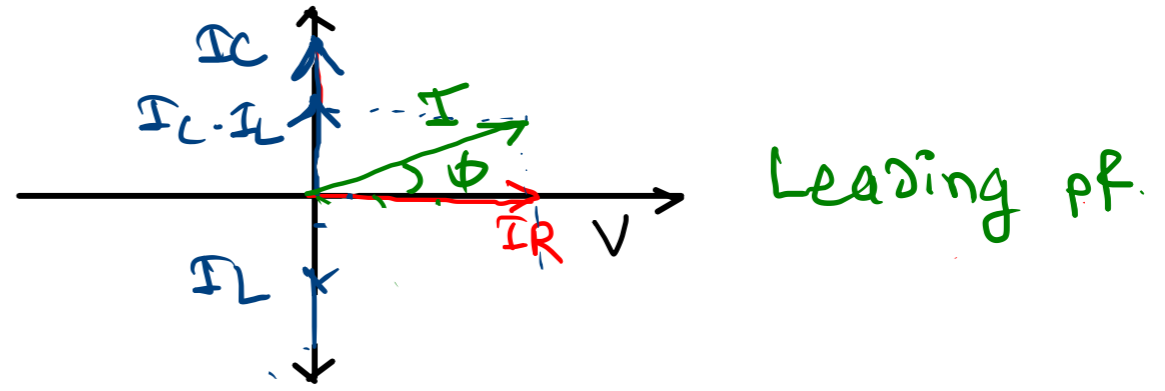

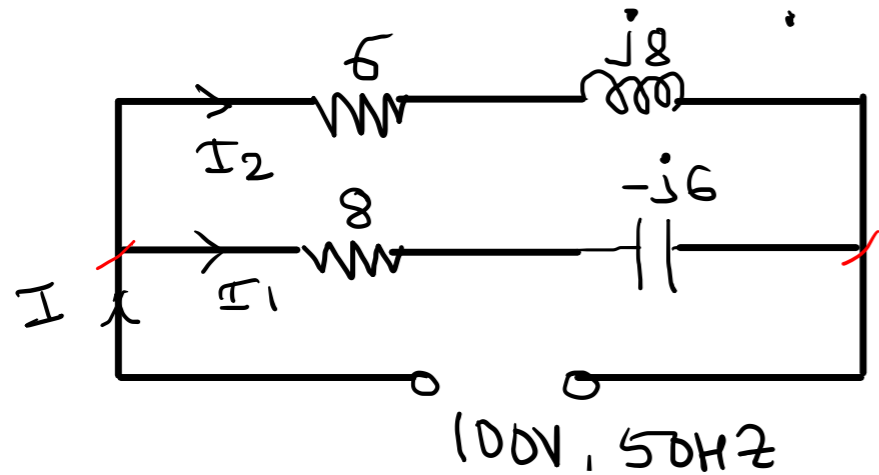1. Find current I_1 and I_2 in the following circuit. Find overall power factor of the circuit, Active power. Draw phasor diagram of the circuit.



$$\Rightarrow Z_1 = (8 - j6)$$


$$Z_2 = (6 + j8)$$

$$\underline{\underline{I = I_1 + I_2}}$$

$$Z = (Z_1 \parallel Z_2)$$

OR

$$Y = Y_1 + Y_2$$

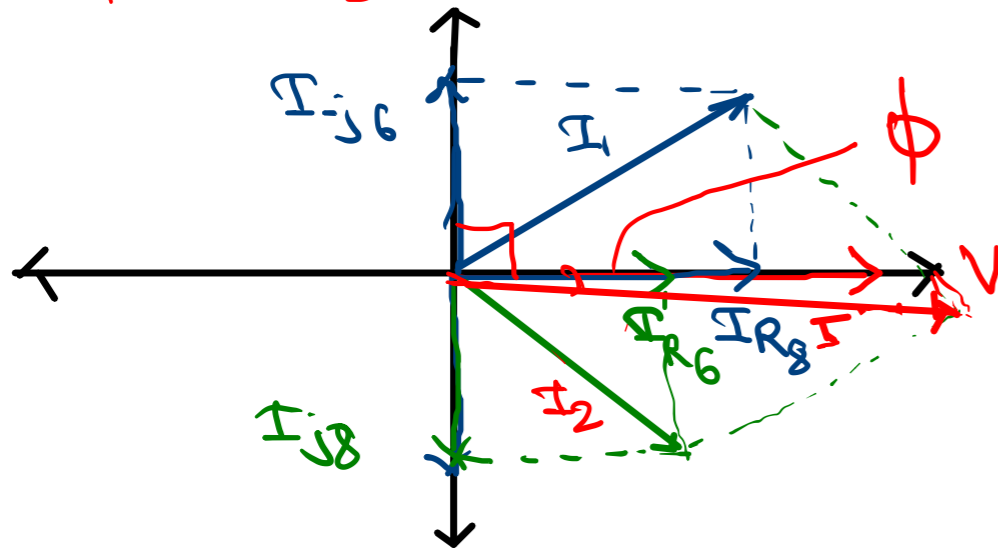

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$Z = \frac{(Z_1 \cdot Z_2)}{(Z_1 + Z_2)}$$

$$Z = \frac{(8 - j6)(6 + j8)}{(8 - j6 + 6 + j8)} = \frac{(10 \angle -36.8^\circ) \times (10 \angle 53.13^\circ)}{14 + j2}$$

$$Z = \frac{100 \angle 16.33^\circ}{14 + j2} = \frac{(95.96 + j28.11)}{14 + j2}$$


$$Z = \frac{100 \angle 16.33^\circ}{14.14 \angle 8.13^\circ} = 7.02 \angle 8.13^\circ$$

$$I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{7.02 \angle 8.13^\circ} = 14.24 \angle -8.13^\circ$$

$$PF = \cos \phi = \cos (8.13^\circ) = 0.98 \text{ (lagging)}$$

$$P_{act} = V_{rms} \times I_{rms} \cos \phi = 100 \times 14.24 \times 0.98 = 1395.5 \text{ Watts}$$

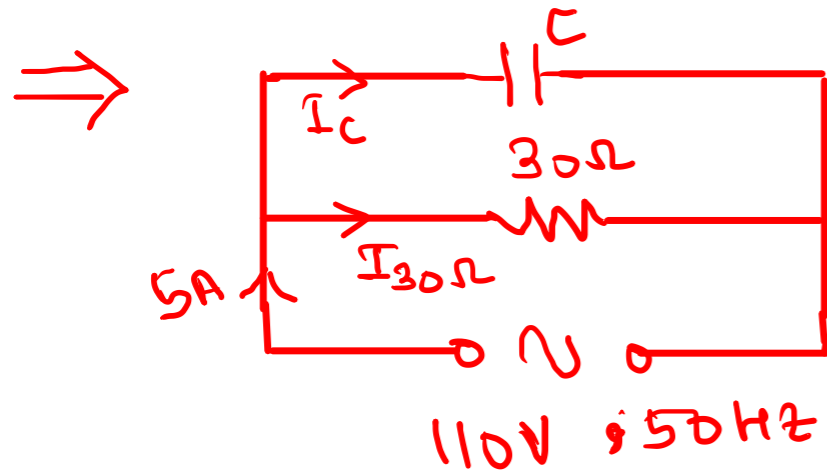2. A resistor of 30 ohm and a capacitor of unknown value are connected in parallel across a 110 V, 50Hz supply. The combination draws a current of 5A from the supply. Find the value of unknown capacitance. The combination is connected across a 110 V supply of unknown frequency, it is observed that total current drawn from the mains falls to 4 A, determine frequency of the supply.



$$I_{30\Omega} = \frac{110}{30} = 3.66 \text{ A}$$

$$\bar{I} = \bar{I}_C + \bar{I}_{30\Omega}$$

$$I^2 = I_C^2 + I_{30\Omega}^2$$

$$I_C^2 = I^2 - I_{30\Omega}^2$$

$$I_C^2 = (5)^2 - (3.66)^2$$

Case-I : $C = ?$ at $I = 5 \text{ A}$

Case-II $f = ?$ at $I = 4 \text{ A}$

$$I_C = 3.4 \text{ A}$$

$$X_C = \frac{V}{I_C} = \frac{110}{3.4}$$

$$X_C = 32.35 \Omega$$

$$X_C = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi \times 50 \times 32.35}$$

$$C = 98.3 \mu\text{F}$$

Case II

$$I = 4 \text{ A}$$

$$I^2 = I_C^2 + I_{30\Omega}^2$$

$$I_C^2 = (4)^2 - (3.66)^2$$


$$I_C = 1.61 \text{ A}$$

$$X_C = \frac{110}{1.61} = 68.32 \Omega$$

$$X_C = \frac{1}{2\pi f C} \text{ , } f = \frac{1}{2\pi \times 68.32 \times 98.3 \times 10^{-6}}$$

$$f = 23.6 \text{ Hz}$$

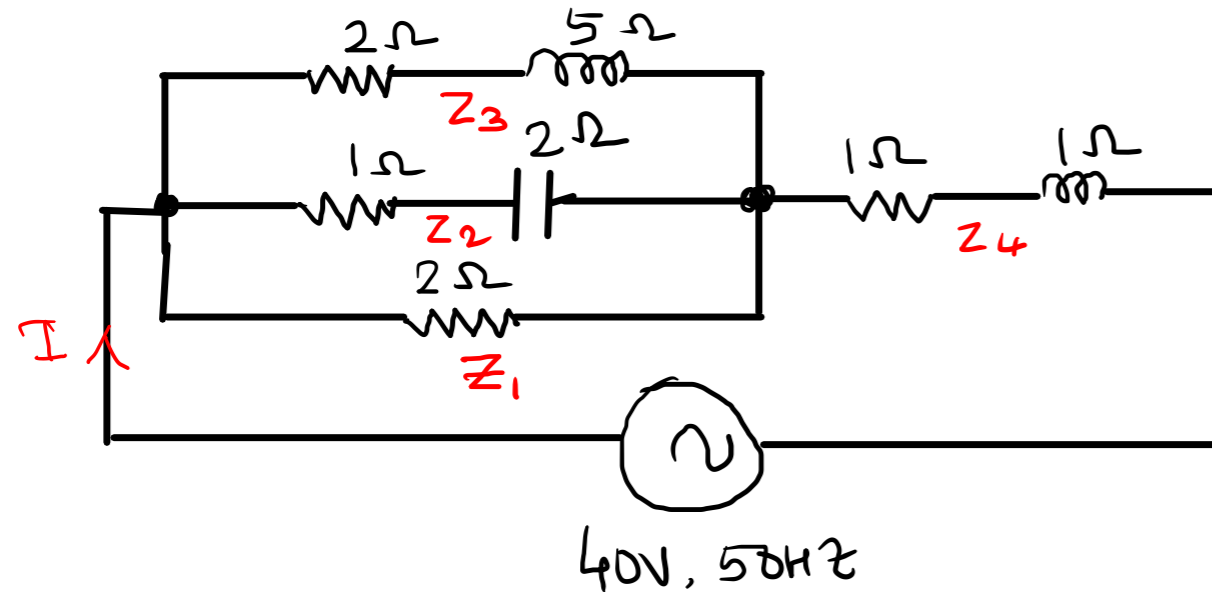3. In the following circuit, calculate i) total impedance (ii) total current (iii) power factor (iv) Active and reactive power.



$$\Rightarrow Z_1 = 2 \Omega, Y_1 = \frac{1}{2} = 0.5 \text{ S}$$

$$Z_2 = 1 - j2, Y_2 = \frac{1}{1 - j2} = 0.2 + j0.4$$

$$Z_3 = 2 + j5, Y_3 = \frac{1}{2 + j5} = 0.068 - j0.17$$

$$Z_4 = 1 + j1$$

$$Y_{123} = Y_1 + Y_2 + Y_3$$

$$Y_{123} = 0.5 + 0.2 + j0.4 + 0.068 - j0.17$$

$$Y_{123} = 0.768 + j0.23$$

$$\therefore Z_{123} = \frac{1}{Y_{123}} = 1.19 - j0.35$$

$$Z = Z_{123} + Z_4$$

$$Z = 1.19 - j0.35 + 1 + j1$$

$$Z = 2.19 + j0.65$$

$$I = \frac{V}{Z} = \frac{40 \angle 0}{2.19 + j0.65} = \frac{40 \angle 0}{2.28 \angle 16.5^\circ}$$

$$I = 17.54 \angle -16.5^\circ$$


$$\text{PF} = \cos \phi = \cos(16.5) = 0.95 (\text{lagging})$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos \phi = 40 \times 17.54 \times 0.95 = 666.5 \text{ Watts}$$

$$Q = V_{\text{rms}} I_{\text{rms}} \sin \phi = 40 \times 17.54 \times \sin(16.5)$$

$$Q = 199.2 \text{ VAR}$$

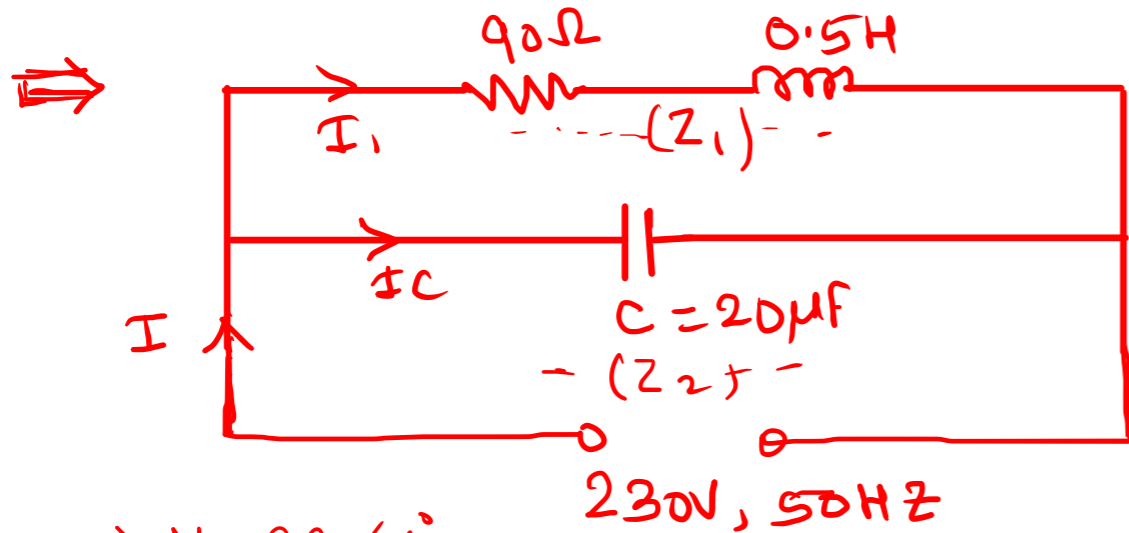4) A series combination of 0.5 H inductor and 90 ohm resistor are connected in parallel across 20 uF. Find (i) the total current (ii) power factor of the circuit (iii) total power taken from the source. Draw phasor diagram. A voltage of 230 V , 50 Hz is maintained across the circuit.




$$\Rightarrow V = 230 \angle 0^\circ$$

$$Z_1 = 90 + j2\pi fL$$

$$Z_1 = 90 + j2\pi \times 50 \times 0.5$$

$$Z_1 = 90 + j50\pi$$

$$Z_1 = 90 + j157$$

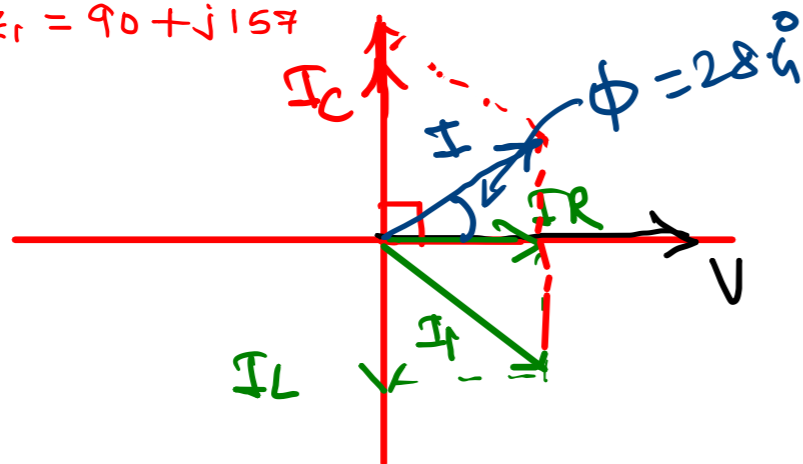

$$I = ? , PF = \cos \phi = ?$$

$$P_{act} = ? \quad \text{phasor diagram}$$

$$Z_2 = \frac{-j}{2\pi fC} = -j \frac{1}{2\pi \times 50 \times 20 \times 10^{-6}}$$

$$Z_2 = (-j159.15) \Omega$$

$$Z = (Z_1) \parallel Z_2 = \frac{(90 + j157) \times (-j159.15)}{90 + j157 - j159.15}$$

$$Z = \frac{(24986.55 - j14323.5)}{(90 - j2.15)}$$

$$Z = (281.26 - j152.43)$$

$$I = \frac{V}{Z} = \frac{230 \angle 0^\circ}{281.26 - j152.13} = 0.71 \angle 28.4^\circ$$

$$PF = \cos \phi = \cos (28.4^\circ) = 0.87 \text{ (leading)}$$

$$P_{act} = V_{rms} I_{rms} \cos \phi = 230 \times 0.71 \times 0.87 = 142.07 \text{ Watts}$$